

# Wish you all Very Happy New Year

## Course: Basic Electronics (EC21101)

Course Instructors:

Prof. Kapil Debnath,

Prof. S. K. Varshney,

Prof. Bratin Ghosh,

Prof. Aniket Singha

MON(10:00-10:55) , WED(08:00-08:55) , WED(09:00-09:55) ,  
THURS(10:00-10:55)

Contact Email: [k.debnath@ece.iitkgp.ac.in](mailto:k.debnath@ece.iitkgp.ac.in)  
website: <https://kdebnath8.wixsite.com/nanophotonics>

Office: R314, ECE Dept, Discussion time: Friday 5pm

# Course Breakup

- **Mid-Semester Examination : 30 Marks**
- **End-Semester Examination: 50 Marks**
- **TA: 20 Marks**
  - Two class Tests (14 marks)
  - Tutorial (3 marks)
  - Attendance and interaction in class (3 marks)

**Mid Semester Examination: 18-26 Feb. 2019**

**End-Semester Examination: 22-30 April 2019**

# Course contents

- Signal, noise, system, RL, RC filter circuit etc.,
- Intrinsic, extrinsic semiconductor, drift & diffusion current, p-n junction, forward bias/ reverse bias, I-V equation (without proof), diode model (ideal, piece wise linear etc), Zener diode characteristics;
- half wave, full wave rectifier, bridge rectifier, ripple, Zener diode circuit (voltage ref, regulation), filter, clipper, clamper, multi diode circuit
- BJT Basics, alpha-beta relation, I-V equation with different regions, DC circuit analysis, common emitter circuit with and without emitter resistor, BJT amplifier, load line, Q point, small signal equivalent circuit, common emitter amplifier (gain, input resistance, output resistance).

# Course contents

- OPAMP basic, virtual ground, ideal properties, inverting, non inverting, buffer, differential amplifier, CMRR (all these with ideal and non ideal OPAMP gain), integrator, differentiator.
- Digital electronics- number system, Digital gates (symbol, truth table), universal gate, sum of product, product of sum, Karnaugh map, RS/D/T Flip Flop.
- MOSFET basic structure, IV equation (no proof) with different regions, depletion mode, enhancement mode, channel length modulation, DC circuit analysis, common source circuit with and without source resistor
- MOSFET amplifier, load line, Q point, small signal equivalent circuit, common source amplifier (gain, input resistance, output resistance).

# Basic Electronics Lab

- Measurement of resistance, classification of capacitors, diode testing
- Familiarization with signal generator, oscilloscope and studies of RC, CR and RL circuits
- Studies of rectifiers and power supply
- Studies of small signal BJT CE amplifiers
- Studies of analog circuits using OP-AMP
- Studies of Logic gates

# References

## TEXT BOOK

- Donald A. Neamen, *Electronic Circuits-Analysis and Design*
- Sedra and Smith, *Microelectronics* **Text book (some portion).**

## Reference BOOK

- Milliman and Halikas, *Integrated Electronics*, **Reference book**
- Raza Vi, *Fundamentals of Microelectronics*, **Reference book**


# Electronics: History & It's Application

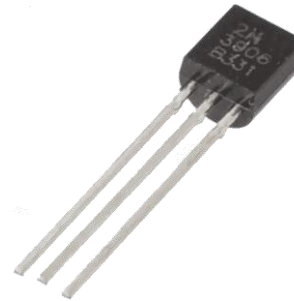**Electronics era came into existence with the invention of vacuum diode in the year 1897.**




Vacuum Diode (1897) – John Ambrose Fleming

Transistor (1948) – John Bardeen, Walter Brattain and William Shockley in Bell Labs (Nobel in 1956)



First transistor

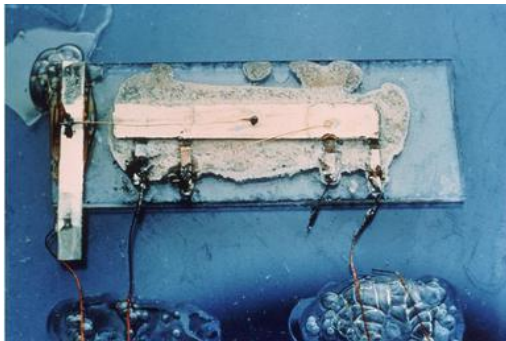


First IC


Integrated Circuit (1958) – Jack Kilby  
(Nobel in 2000)

# Electronics: History & It's Application

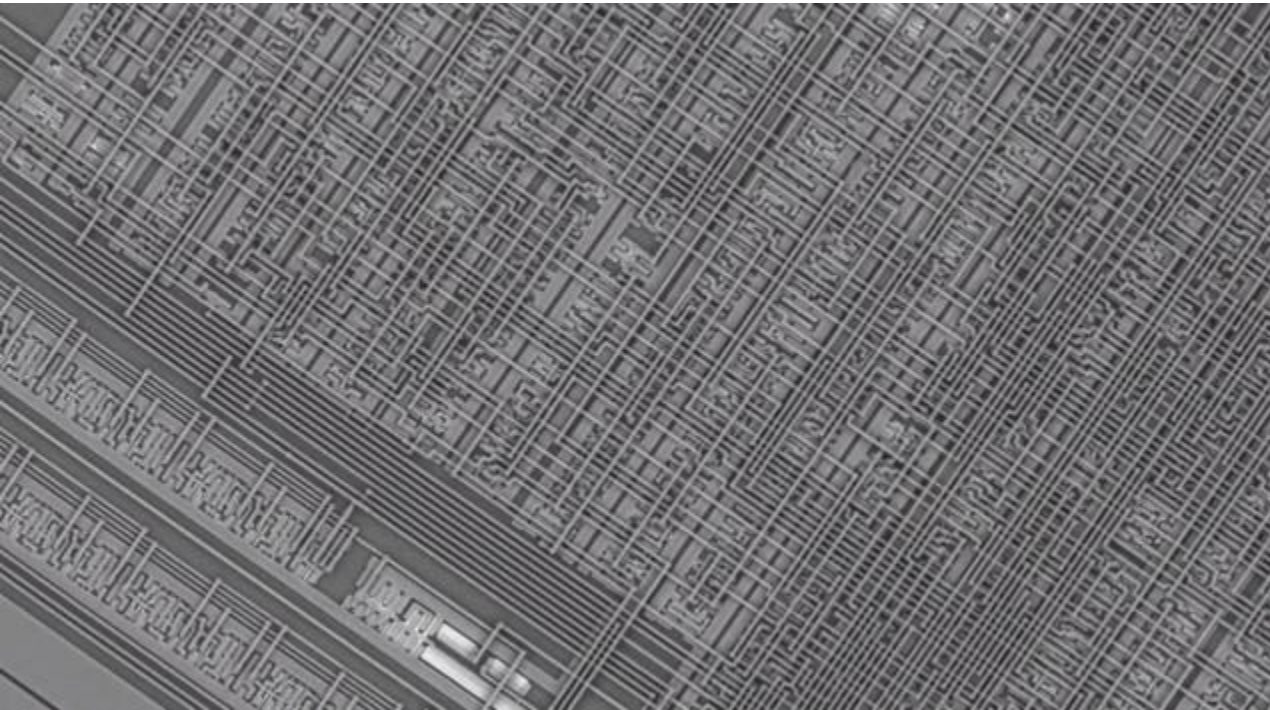**Billions of transistors in a single chip**



Top view (SEM) of an IC chip

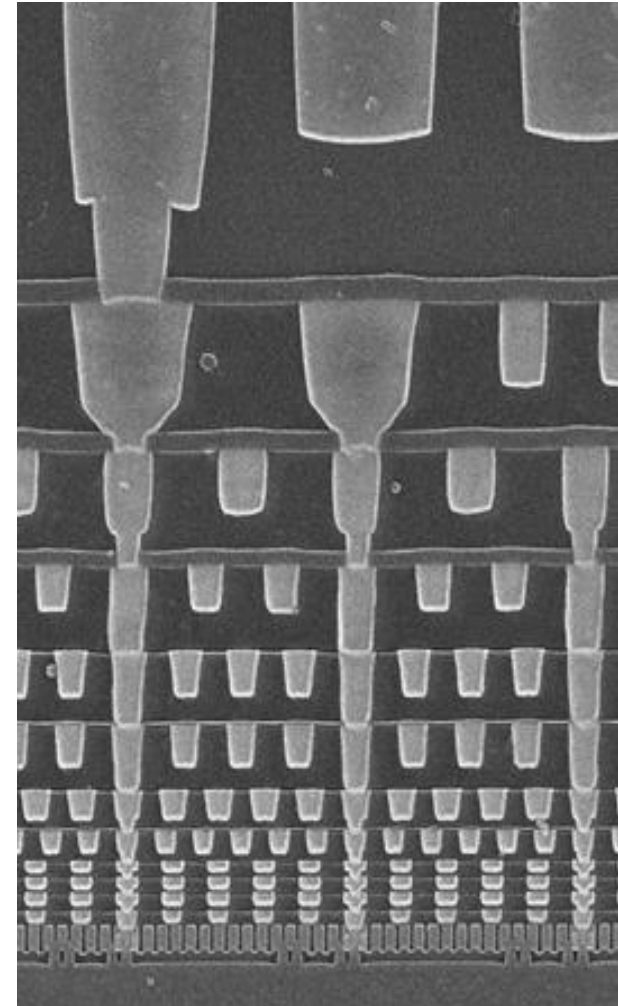


Cross-section view (SEM)  
of an IC chip



# Electronics: History & It's Application



Consumer Electronics

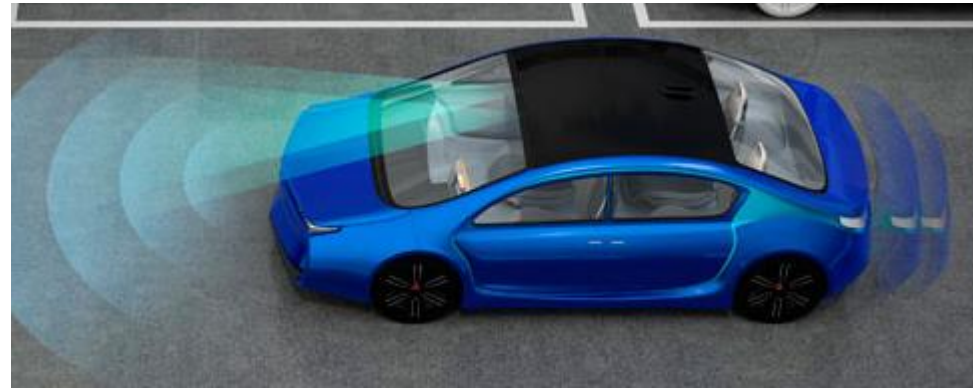

autonomous vehicle



Defence and Aerospace



Communication



Metrology & Sensing

# Electronics Application: Example

## Cell Phone charger



# Electronics Application: Example

## Cell Phone charger

Line voltage : 220V 50Hz




Cell Battery: 3.7V

*Can you build a charger with known electrical components, e.g. resistor, capacitor and inductor?*

# Electronics Application: Example

## Cell Phone charger

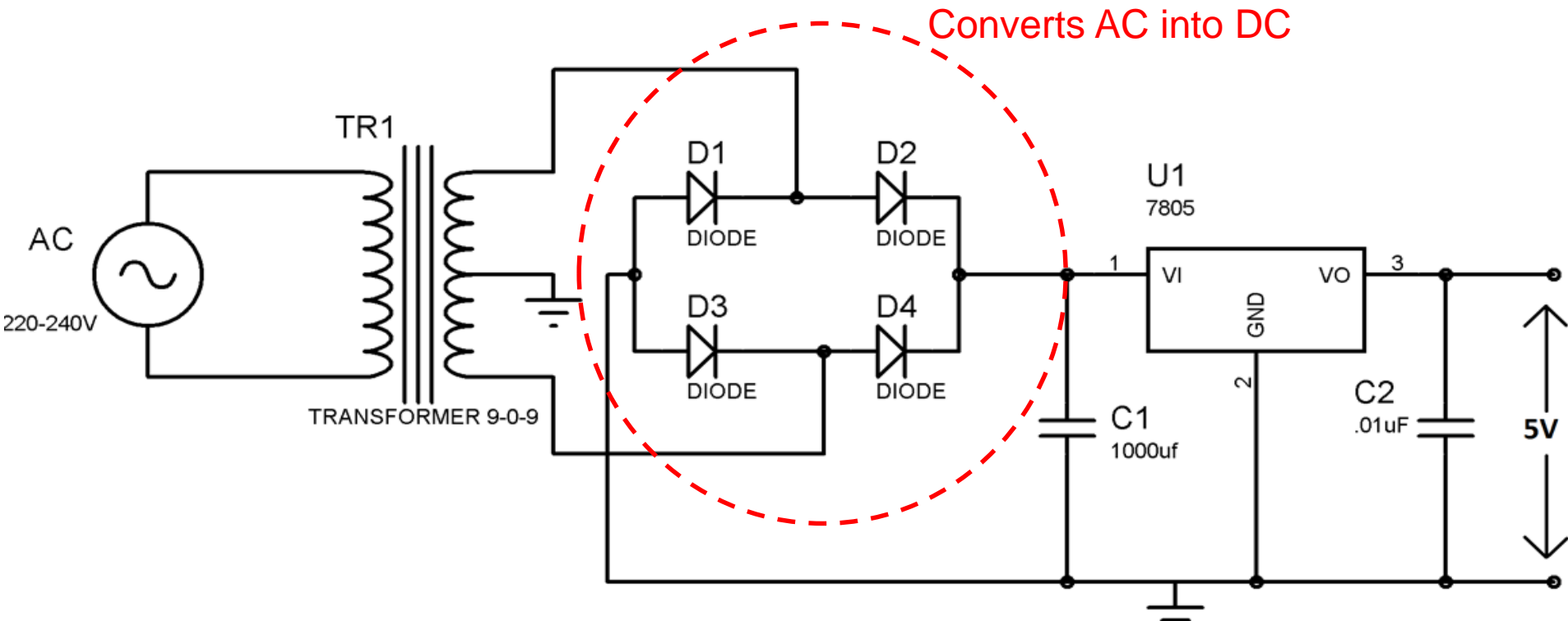

# Components of an Electronics Circuit


Image

Symbol


**Resistor**



**Inductor**

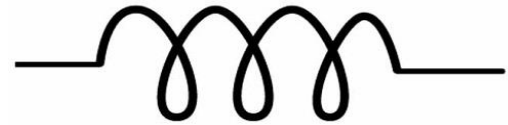

**Capacitor**


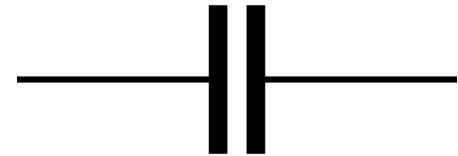


# Components of an Electronics Circuit


Image

Symbol

**Diode**

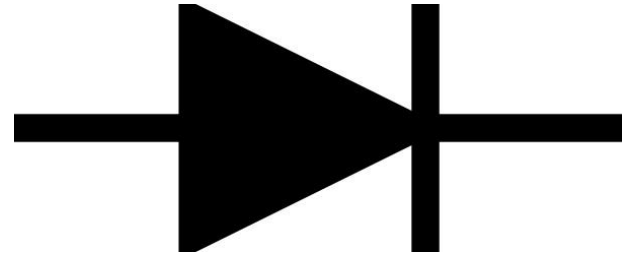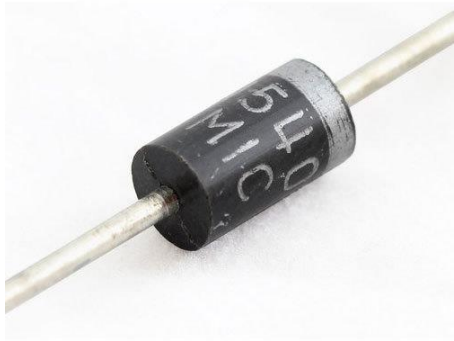

**Transistor**

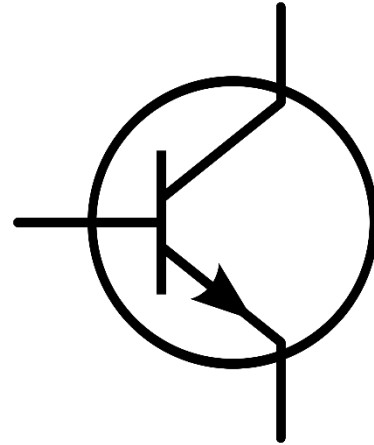

# Components of an Electronics Circuit

**Passive components:** components which can not supply energy to the circuit themselves.

Resistor, Capacitor, Inductor etc.


**Active components:** components which can supply energy to the circuit or control the energy flow.

Battery, Transistor, AC signal generator, Diode etc.




# Electronic System

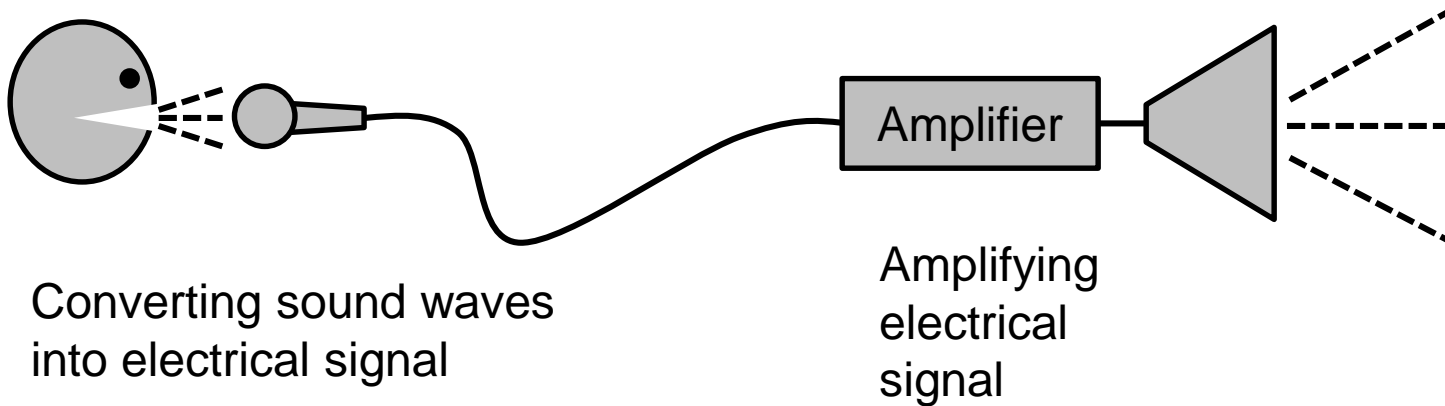**Consists of multiple passive and active components to alter or modify an incoming electrical signal**





# Electronic System

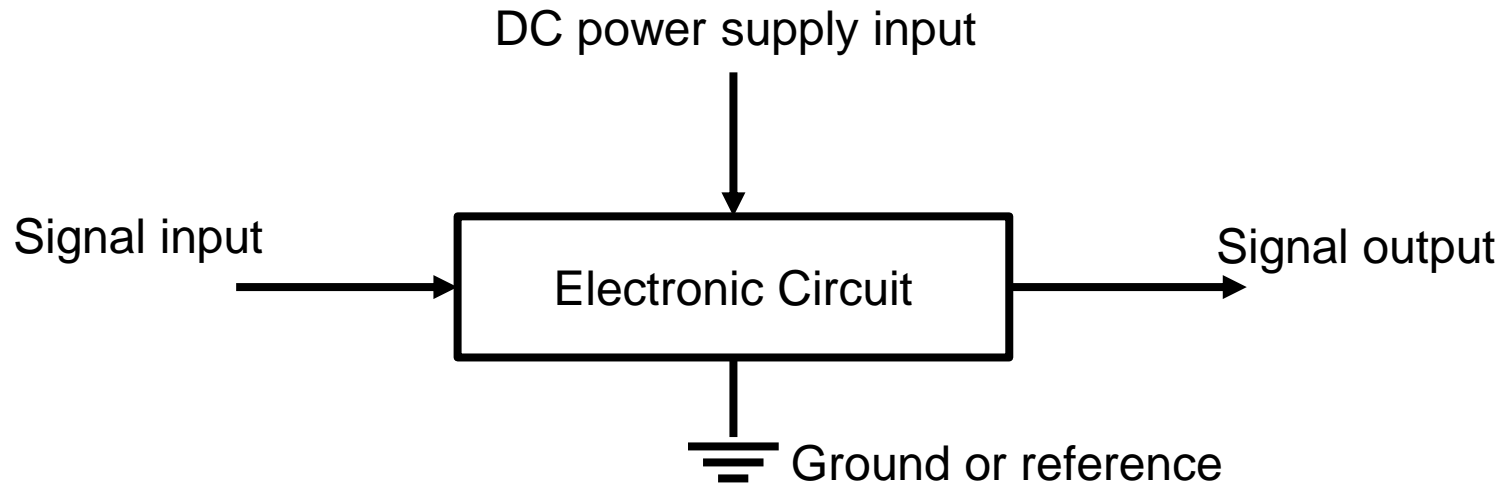

## **Analog Electronic Circuit:**


The signals are continuously variable



Voice signal
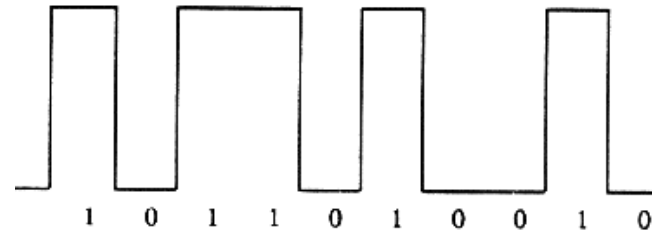
## **Digital Electronic Circuit:**

The signals usually takes two or more levels




Binary signal

# Circuits with passive components


## Current-voltage relationship

Resistor

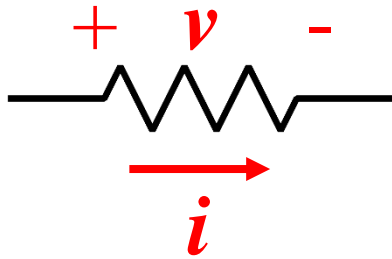


$$v = iR$$

Capacitor

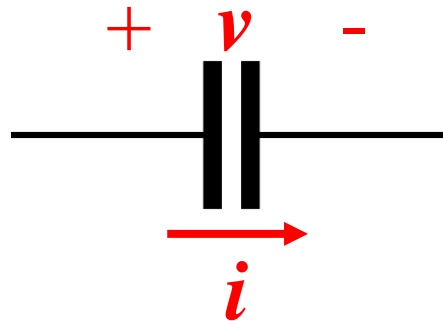

$$i = C \frac{dv}{dt}$$

Inductor

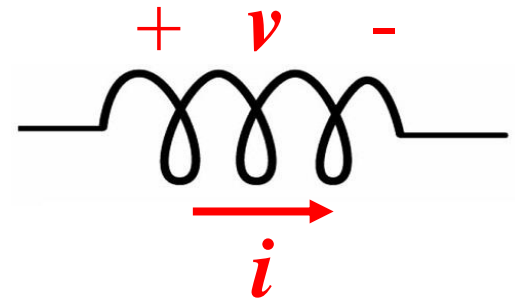


$$v = L \frac{di}{dt}$$


# Circuits with passive components

## Impedance


### Resistor

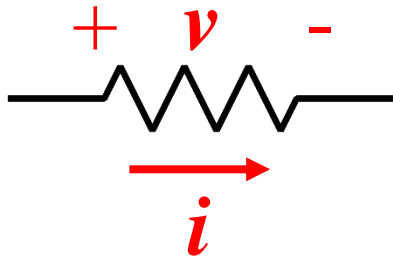


$$Z_R = R$$

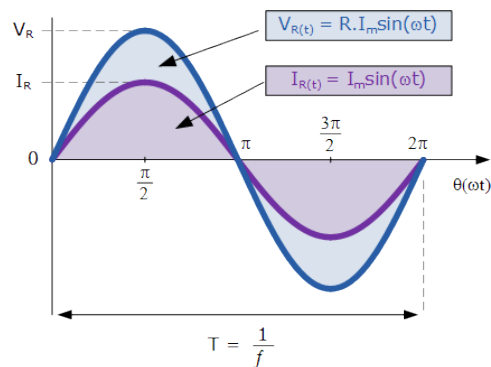


### Capacitor

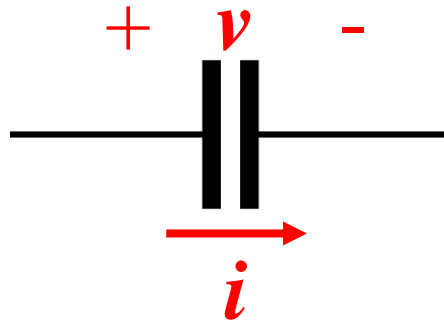


$$Z_C = -j \frac{1}{\omega C}$$

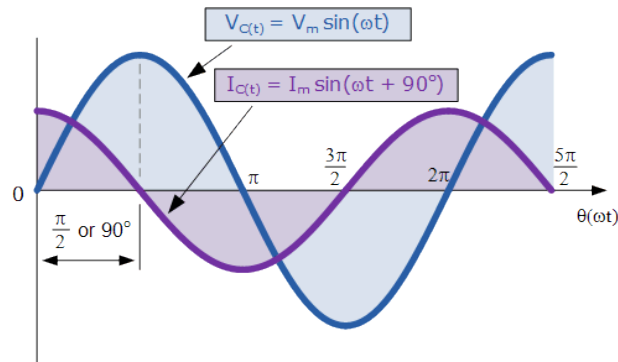

### Inductor

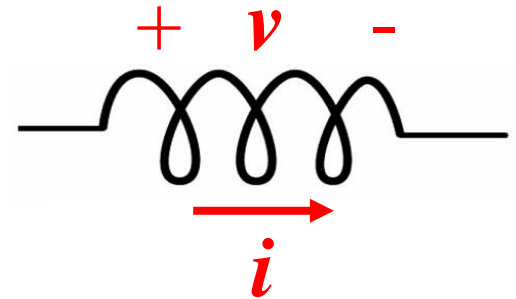


$$Z_L = j\omega L$$

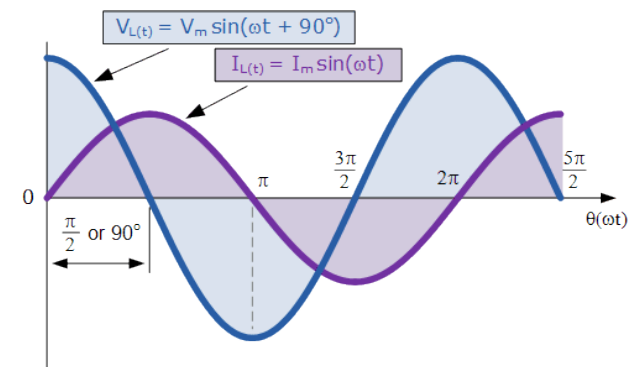

# Kirchhoffs Circuit Law
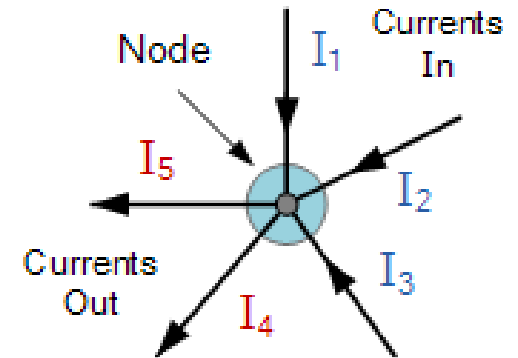
## Kirchhoffs Current Law


Currents Entering the Node  
Equals  
Currents Leaving the Node



$$I_1 + I_2 + I_3 + (-I_4 + -I_5) = 0$$
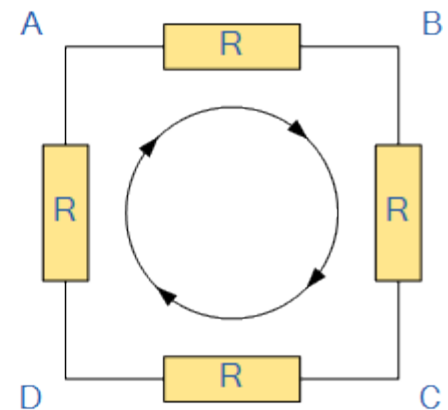
## Kirchhoffs Voltage Law


The sum of all the Voltage  
Drops around the loop  
is equal to Zero



$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$

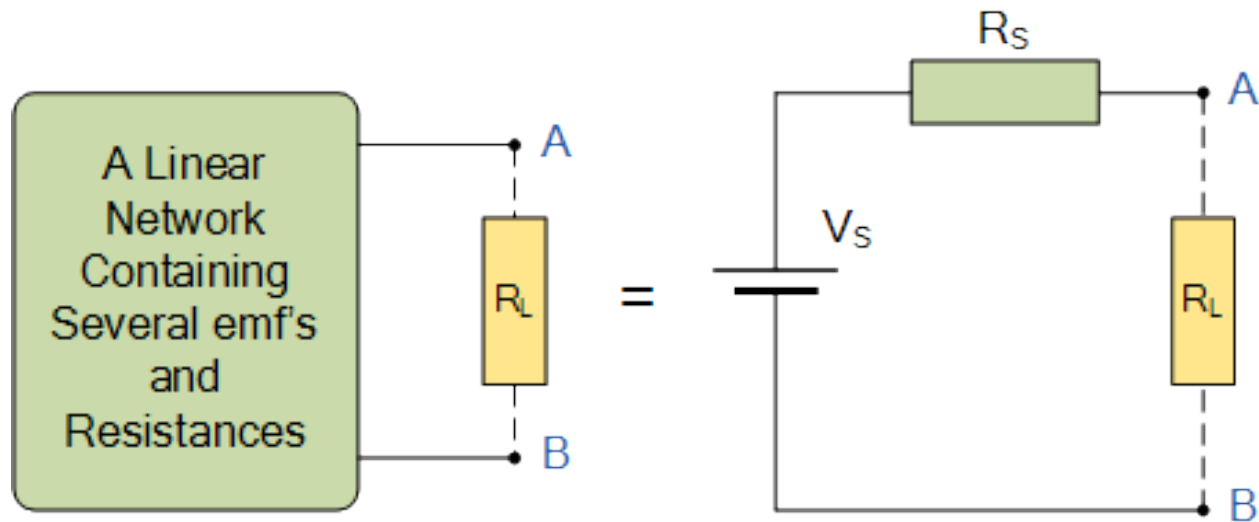
# Thevenin's theorem

*Any linear circuit containing several voltage sources and impedances can be replaced by just one single voltage source in series with a single impedance connected across the load*



# Thevenin's theorem

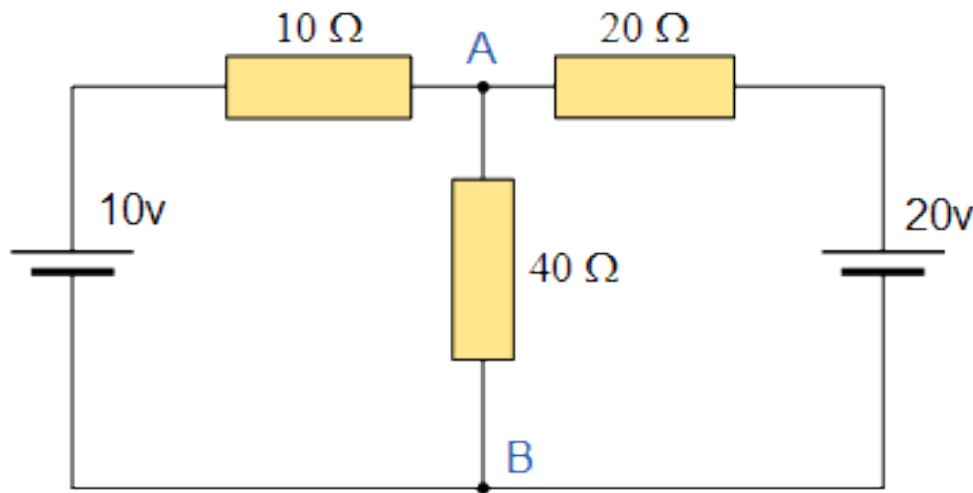**Example:** consider the following circuit. Find out the voltage across the load resistance ( $40\Omega$ ) using Thevenin's theorem



**Ans: 13.33V**


**Step1:** The value of the equivalent resistance,  $R_s$  is found by calculating the total resistance looking back from the terminals A and B with all the voltage sources shorted. We then get the following circuit.

**Step2:** The value of the equivalent resistance,  $V_s$  can be found disconnecting the load resistance and calculating the open circuit voltage between AB.

# R,L,C Filter circuits


Filter circuits are used to remove unwanted frequency components (noise) from an input signal

Ideal filter response:

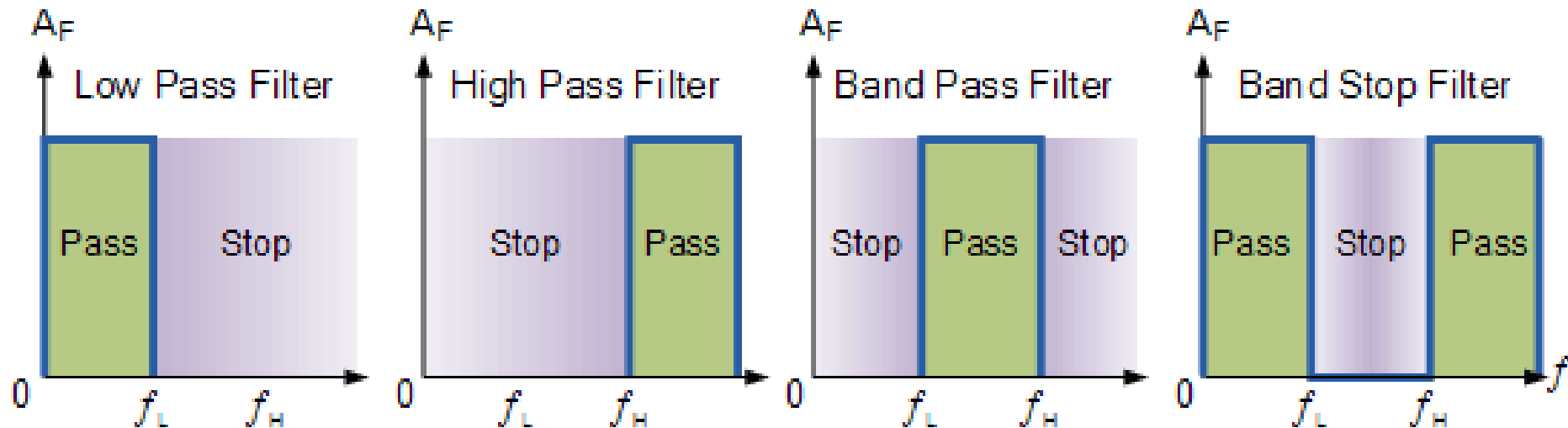

# R,L,C Filter circuits

## Example

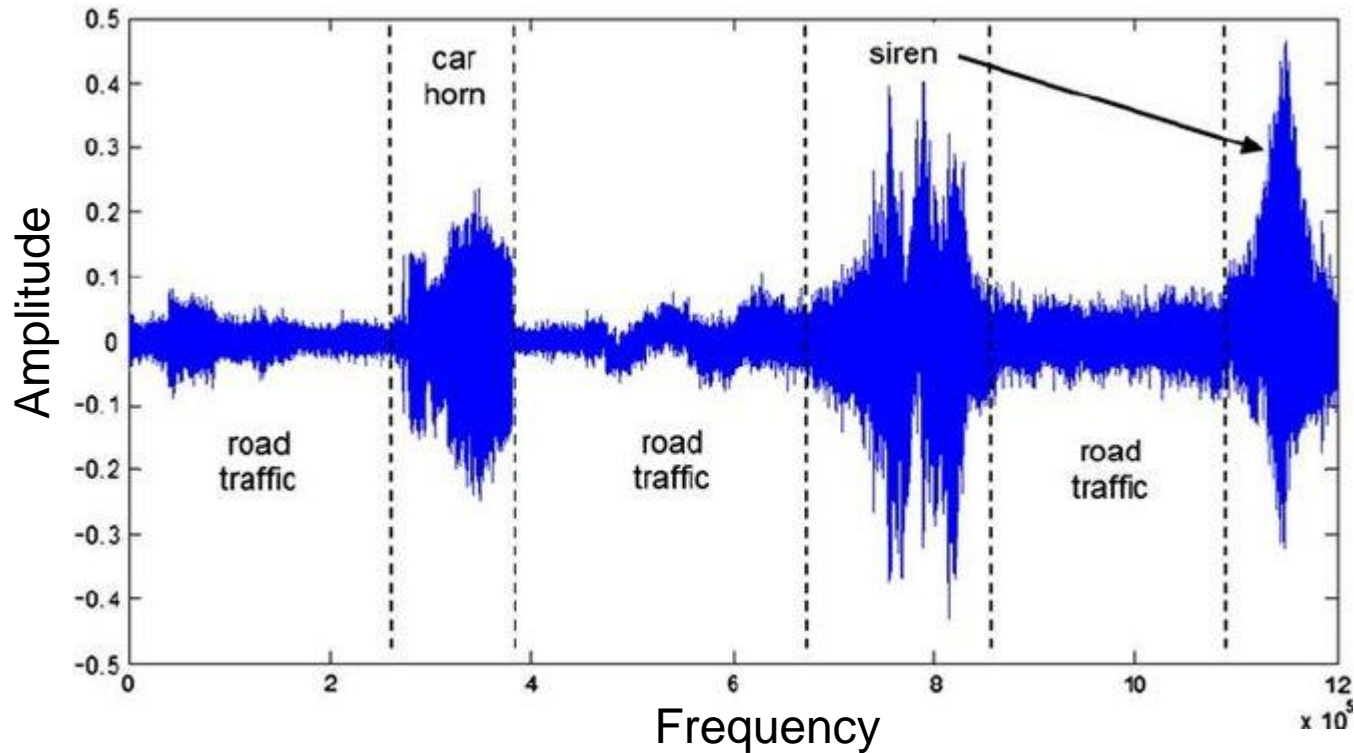


To retain only the sound of the siren from the audio signal we can use a high pass filter




# R,L,C Filter circuits
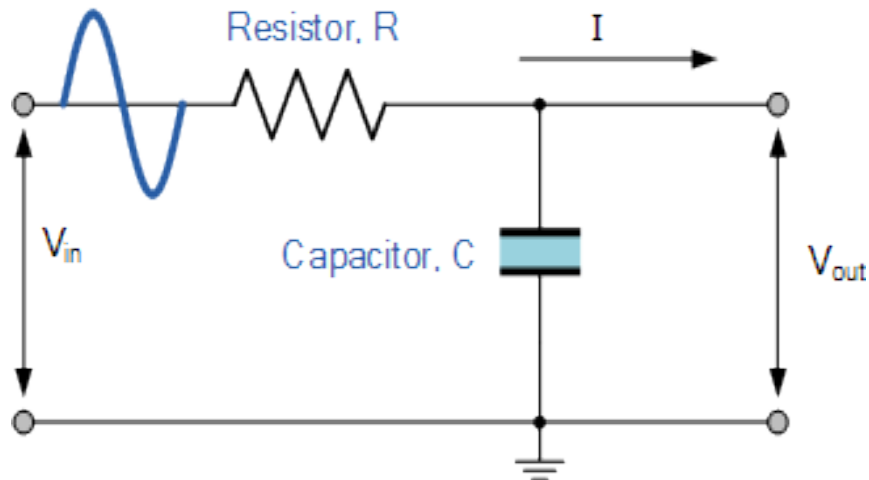
## RC Circuit

Low pass filter: Blocks high frequency signals



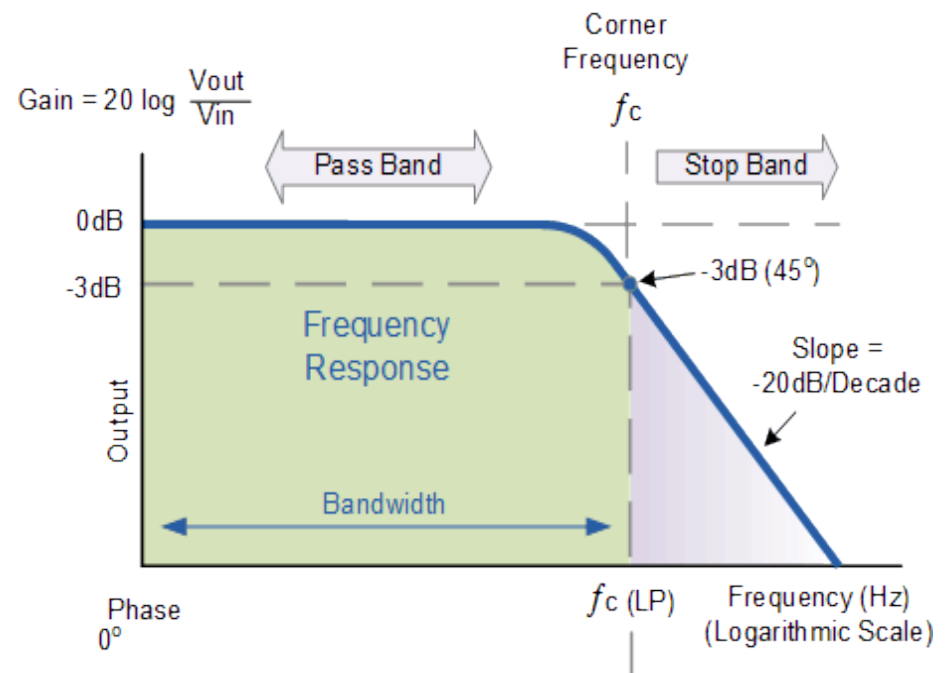
$$V_{out} = \frac{1}{j\omega RC + 1} V_{in}$$




# R,L,C Filter circuits

## RC Circuit

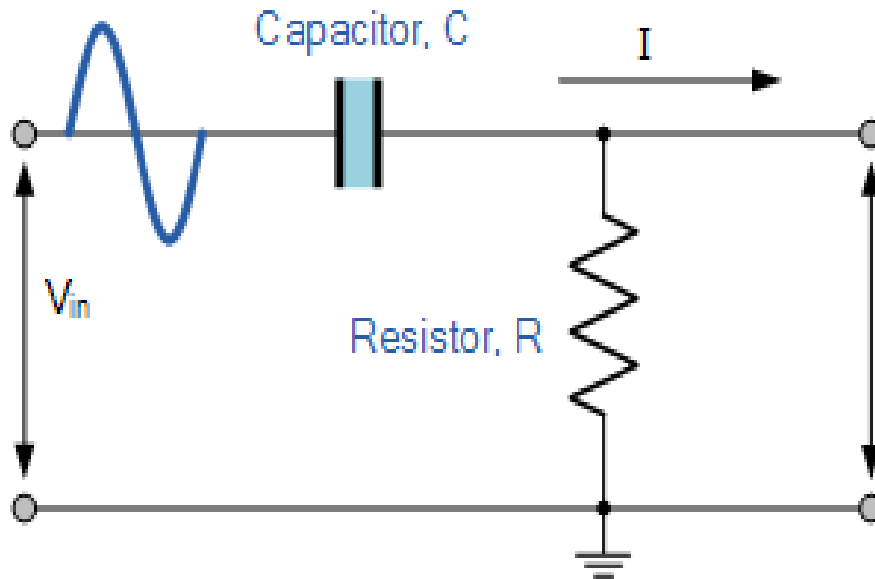**High pass filter: Blocks low frequency signals**





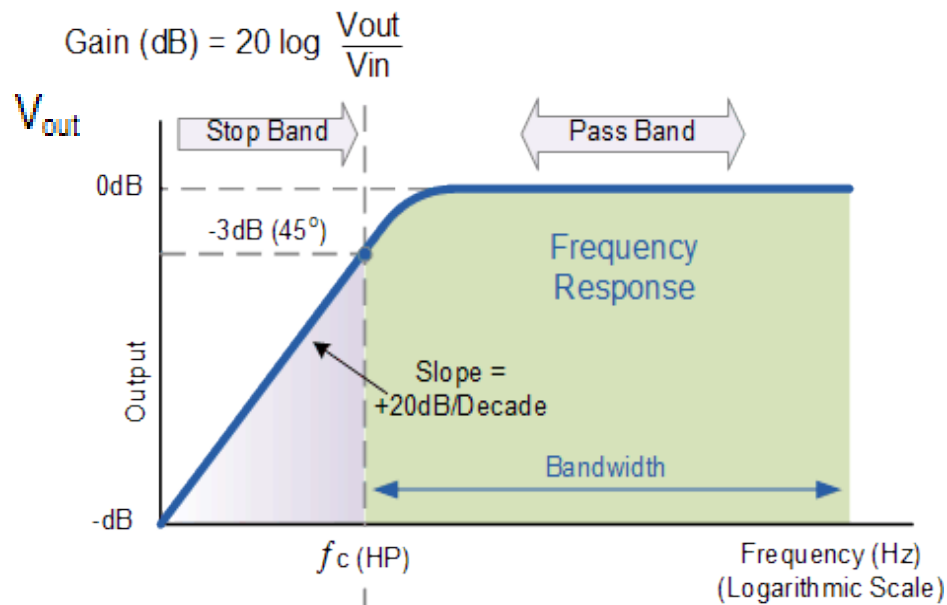
$$V_{out} = \frac{j\omega RC}{j\omega RC + 1} V_{in}$$




# R,L,C Filter circuits

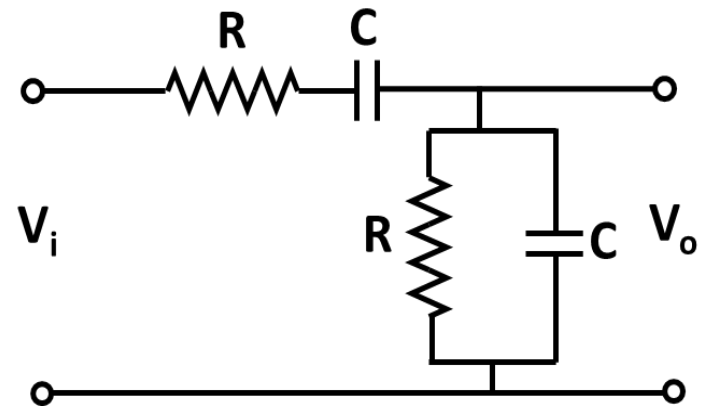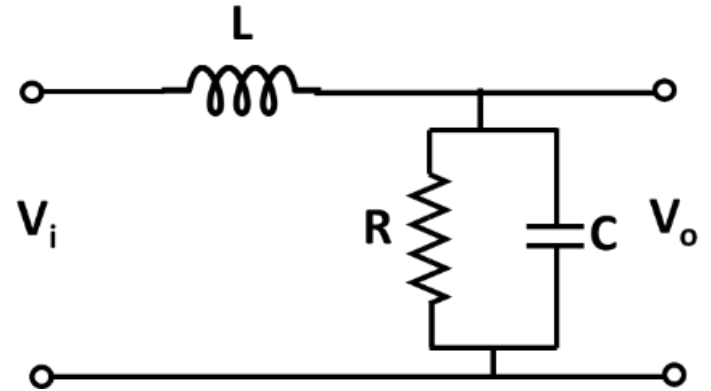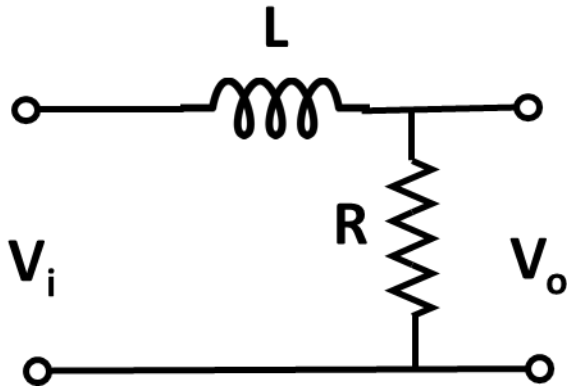**Exercise: What type of filters are the following circuits**


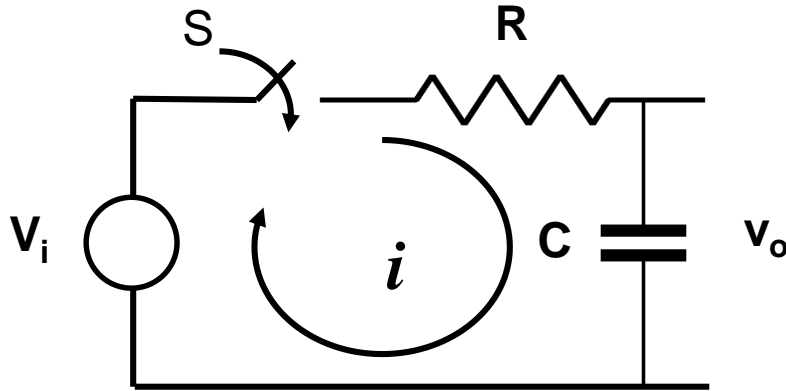
# Transient Response of an RC circuits

Consider  $V_i$  is a DC voltage source connected in series with a resistance  $R$  and a capacitance  $C$  through a switch. If at time  $t=0$ , the switch is closed, then what would be the voltage across the capacitor and the current through it?



Current through C:

$$i(t) = C \frac{dv_o}{dt}$$

Using KVL in the circuit:

$$V_i = v_R + v_o$$


$$\Rightarrow V_i = iR + v_o$$

$$\Rightarrow V_i = RC \frac{dv_o}{dt} + v_o$$

Solution to this non-homogeneous ordinary differential equation is


$$v_o = V_i(1 - e^{-t/RC})$$

$$i = \frac{V_i}{R} e^{-t/RC}$$

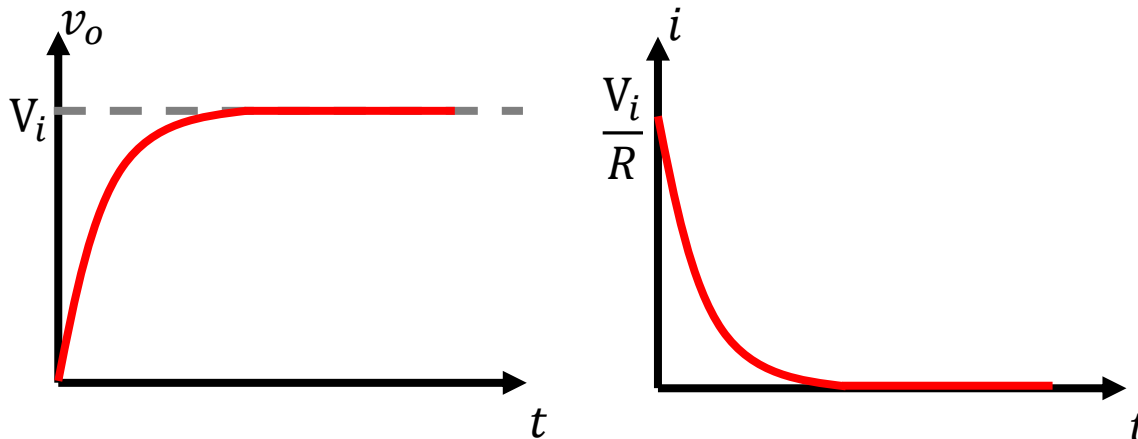


How does  $RC$  effect the response?

# RC Circuit as integrator

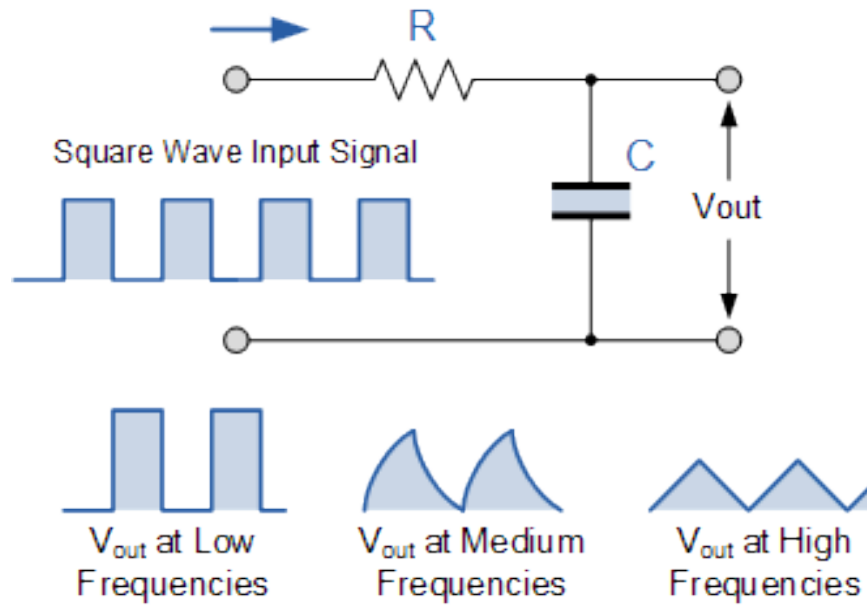

$$V_{OUT} = \frac{1}{RC} \int_0^t V_{IN(t)} dt$$

# RC Circuit as Differentiator

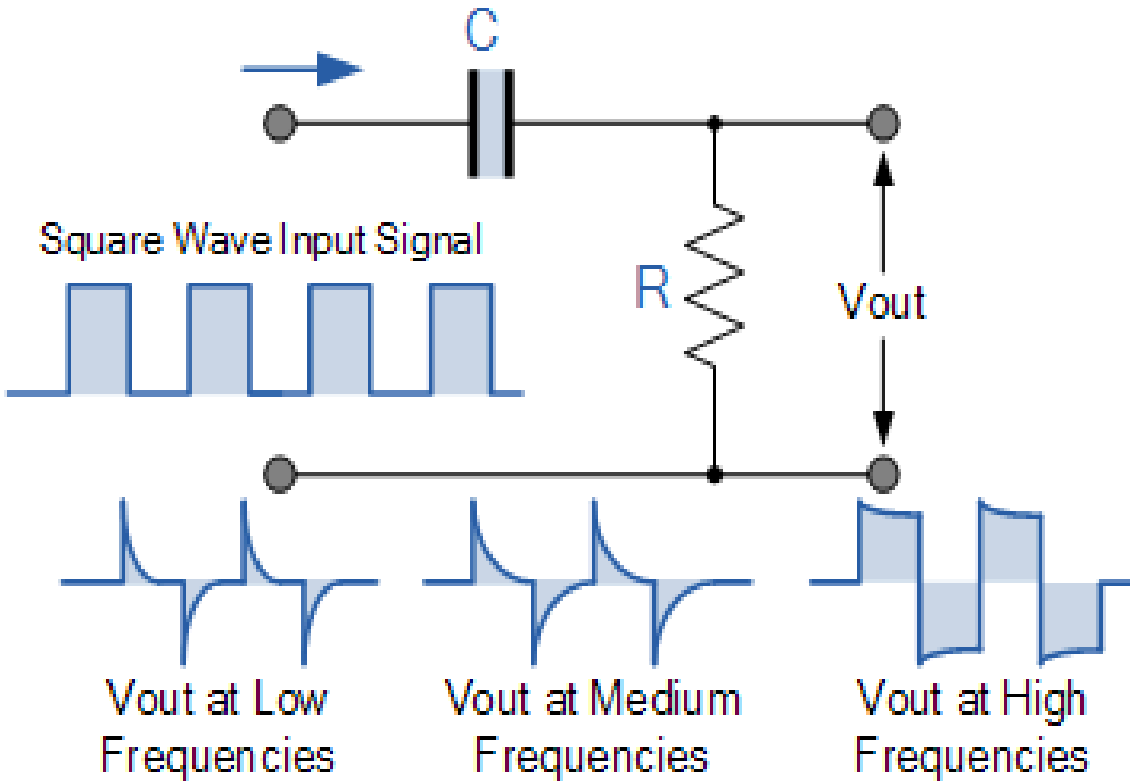

$$V_{OUT} = RC \frac{dV_{IN}}{dt}$$