

- 2.7 The full-wave rectifier circuit shown in Figure P2.7 has an input signal whose frequency is 60 Hz. The rms value of $v_s = 8.5$ V. Assume each diode cut-in voltage is $V_\gamma = 0.7$ V. (a) What is the maximum value of V_O ? (b) If $R = 10\ \Omega$, determine the value of C such that the ripple voltage is no larger than 0.25 V. (c) What must be the PIV rating of each diode?

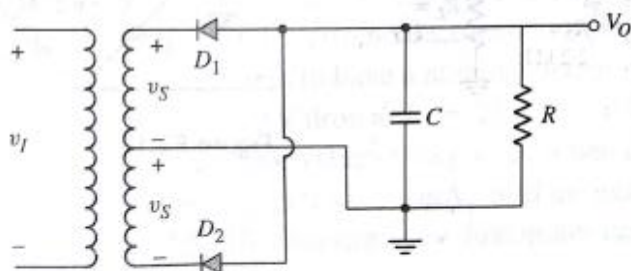


Figure P2.7

- 2.9 The circuit in Figure P2.9 is a complementary output rectifier. If $v_s = 26 \sin [2\pi(60)t]$ V, sketch the output waveforms v_o^+ and v_o^- versus time, assuming $V_\gamma = 0.6$ V for each diode.

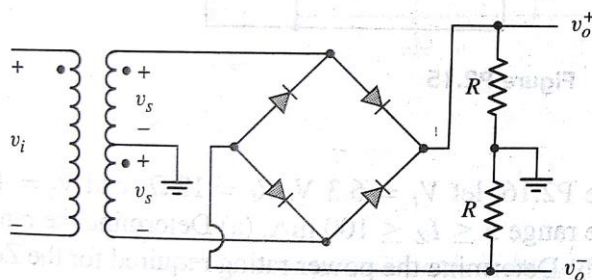


Figure P2.9

- *2.13 (a) Sketch v_o versus time for the circuit in Figure P2.13. The input is a sine wave given by $v_i = 10 \sin \omega t$ V. Assume $V_\gamma = 0$. (b) Determine the rms value of the output voltage.

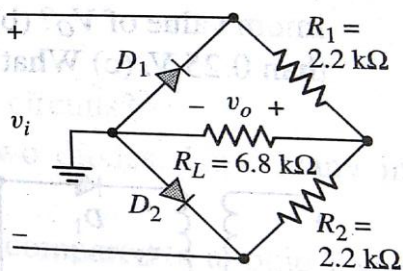


Figure P2.13

- *2.21 A voltage regulator is to have a nominal output voltage of 10 V. The specified Zener diode has a rating of 1 W, has a 10 V drop at $I_Z = 25$ mA, and has a Zener resistance of $r_z = 5\ \Omega$. The input power supply has a nominal value of $V_{PS} = 20$ V and can vary by ± 25 percent. The output load current is to vary between $I_L = 0$ and 20 mA. (a) If the minimum Zener current is to be $I_Z = 5$ mA, determine the required R_i . (b) Determine the maximum variation in output voltage. (c) Determine the percent regulation.
- 2.22 Consider the circuit in Figure P2.22. Let $V_\gamma = 0$. The secondary voltage is given by $v_s = V_s \sin \omega t$, where $V_s = 24$ V. The Zener diode has parameters $V_Z = 16$ V at $I_Z = 40$ mA and $r_z = 2\ \Omega$. Determine R_i such that the load current can vary over the range $40 \leq I_L \leq 400$ mA with $I_Z(\min) = 40$ mA and find C such that the ripple voltage is no larger than 1 V.

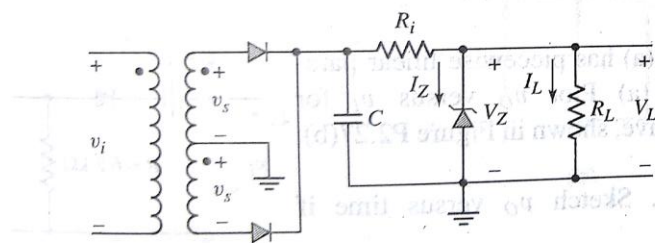


Figure P2.22

- 2.27 The diode in the circuit of Figure P2.27(a) has piecewise linear parameters $V_\gamma = 0.7$ V and $r_f = 10\ \Omega$. (a) Plot v_O versus v_I for $-30 \leq v_I \leq 30$ V. (b) If the triangular wave, shown in Figure P2.27(b), is applied, plot the output versus time.

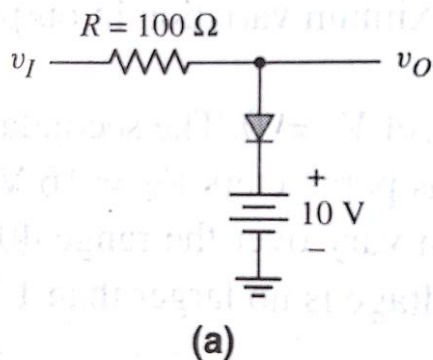


Figure P2.27

- 2.39 The diodes in the circuit in Figure P2.39 have the same piecewise linear parameters as described in Problem 2.37. Determine the output voltage V_O and the currents I_{D1} , I_{D2} , I_{D3} , and I for the following input conditions: (a) $V_1 = V_2 = 0$; (b) $V_1 = V_2 = 5$ V; (c) $V_1 = 5$ V, $V_2 = 0$; and (d) $V_1 = 5$ V, $V_2 = 2$ V.

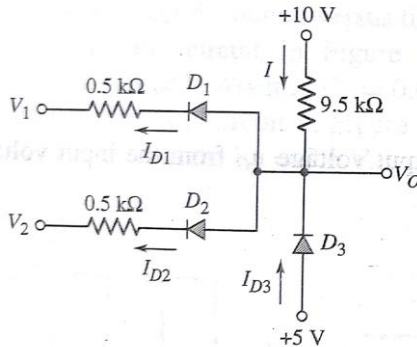


Figure P2.39

- 2.41 (a) For the circuit in Figure P2.41, each diode has $V_\gamma = 0.6$ V. Plot v_O versus v_I over the range $0 \leq v_I \leq 10$ V. (b) Compare the results of part (a) with a computer simulation analysis.

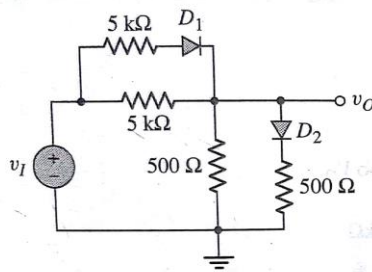


Figure P2.41

- *2.42 Assume $V_\gamma = 0.7$ V for each diode in the circuit in Figure P2.42. Plot v_O versus v_I for $-10 \leq v_I \leq +10$ V.

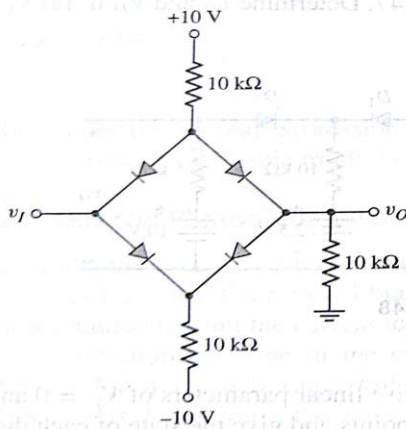


Figure P2.42