

1. The applied electric field in p-type silicon is $E = 15 \text{ V/cm}$. The semiconductor conductivity is $\sigma = 2.2 (\Omega - \text{cm})^{-1}$ and the cross sectional area is $A = 10^{-4} \text{ cm}^2$. Determine the drift current in the semiconductor.
2. The required conductivity of a semiconductor material must be $\sigma = 0.5 (\Omega - \text{cm})^{-1}$. What must be the concentration of donor impurities in the semiconductor?
3. The hole concentration in the semiconductor is given by

$$p(x) = 10^4 + 10^{15} \exp\left(-\frac{x}{L_p}\right) \quad x \geq 0$$

The value of L_p is $10 \mu\text{m}$. The hole diffusion coefficient is $D_p = 15 \text{ cm}^2/\text{s}$. Determine the hole diffusion current density at (a) $x = 0$, (b) $x = 10 \mu\text{m}$ and (c) $x = 30 \mu\text{m}$.

4. The cut-in voltage of the diode shown in the circuit in the Figure 1 is $V_\gamma = 0.7 \text{ V}$. The diode is to remain biased "on" for a power supply voltage in the range $5 \leq V_{PS} \leq 10 \text{ V}$. The minimum diode current is to be $I_{D(\min)} = 2 \text{ mA}$. The maximum power dissipated in the diode is to be no more than 10 mW . Determine appropriate values of R_1 and R_2 .

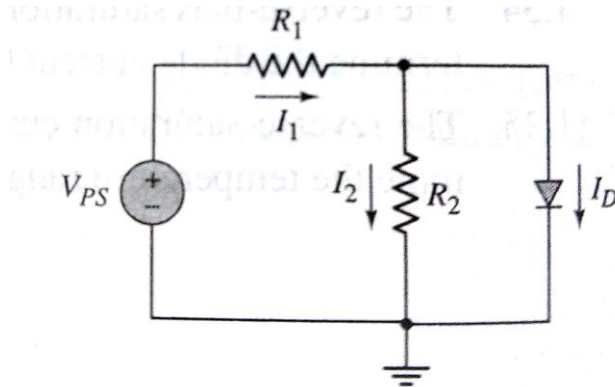


Fig.1

5. Assume each diode in the circuit shown in the Figure 2 has a cut-in voltage of $V_\gamma = 0.65 \text{ V}$. (a) The input voltage is $V_I = 5 \text{ V}$. Determine the value of R_1 required such that I_{D1} is one-half the value of I_{D2} . What are the values of I_{D1} and I_{D2} ? (b) If $V_I = 8 \text{ V}$ and $R_1 = 2 \text{ k}\Omega$, determine I_{D1} and I_{D2} .

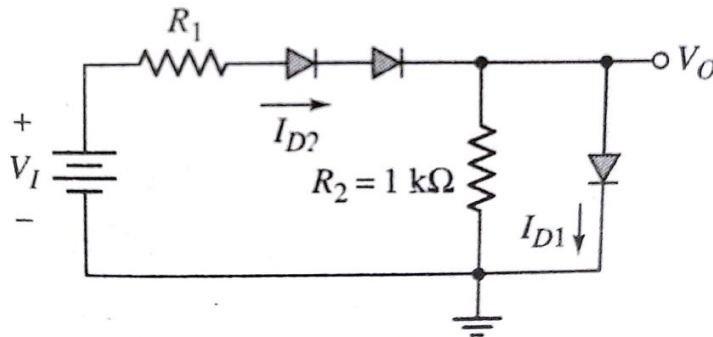


Fig.2

6. The diode in the circuit shown in the Figure 3 is biased with a constant current source I . A sinusoidal signal v_s is coupled through R_S and C . Assume that C is large so that it acts as a short circuit to the signal. (a) Show that the sinusoidal component of the diode voltage is given by $v_0 = v_s \left(\frac{V_T}{V_T + IR_S} \right)$.

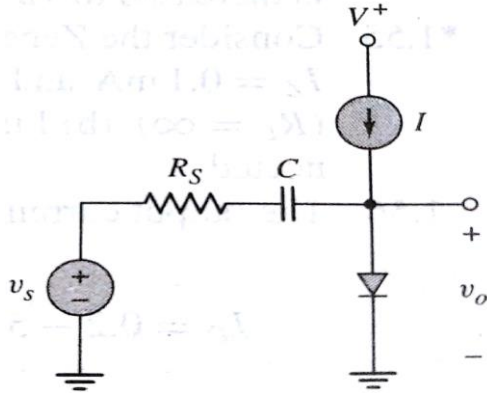


Fig.3

7. Consider the Zener diode circuit shown in Figure 4. The Zener breakdown voltage is $V_Z = 5.6 V$ at $I_Z = 0.1 mA$, and the incremental Zener resistance is $r_z = 10 \Omega$. (a) Determine V_O with no load ($R_L = \infty$) (b) Find the change in the output voltage if V_{PS} changes by $\pm 1V$. (c) Find V_O if $V_{PS} = 10 V$ and $R_L = 2 k\Omega$.

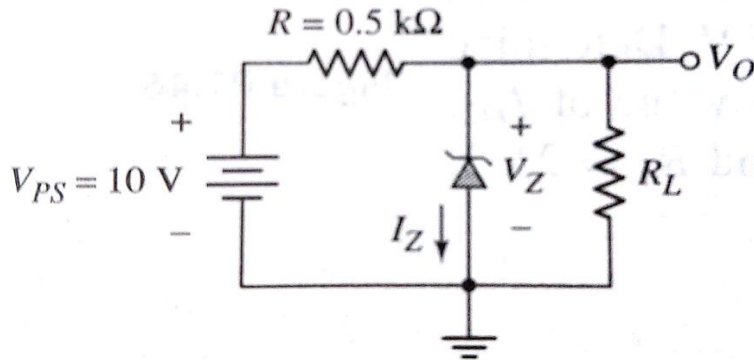


Fig.4

8. Design a circuit to produce the characteristics shown in figure, where v_o is an output voltage and v_i is the input voltage.

