

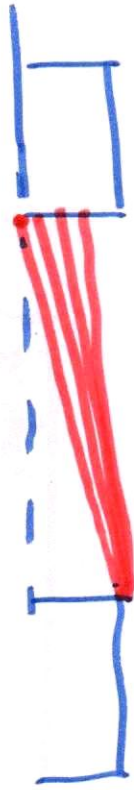




Channel \rightarrow tapered

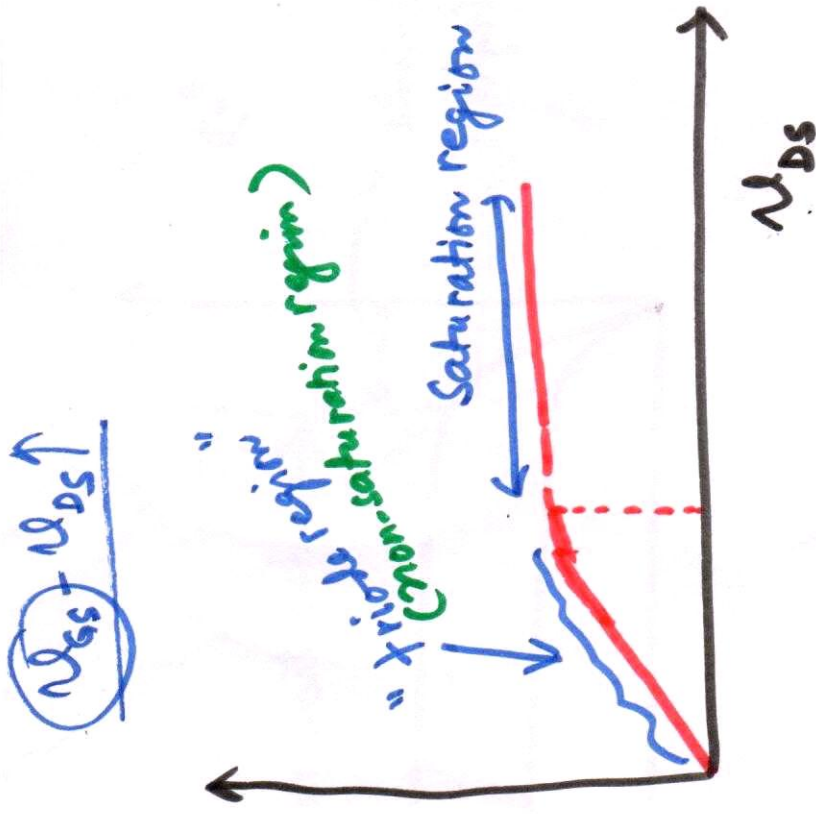

pinch-off region

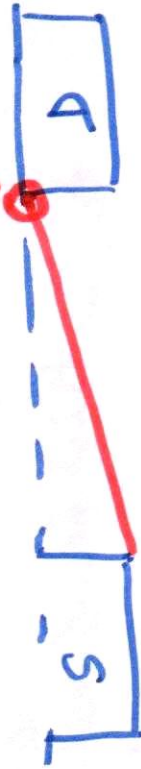

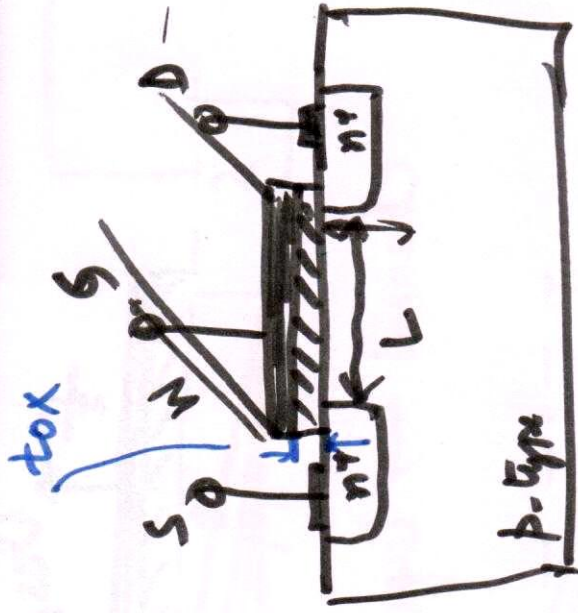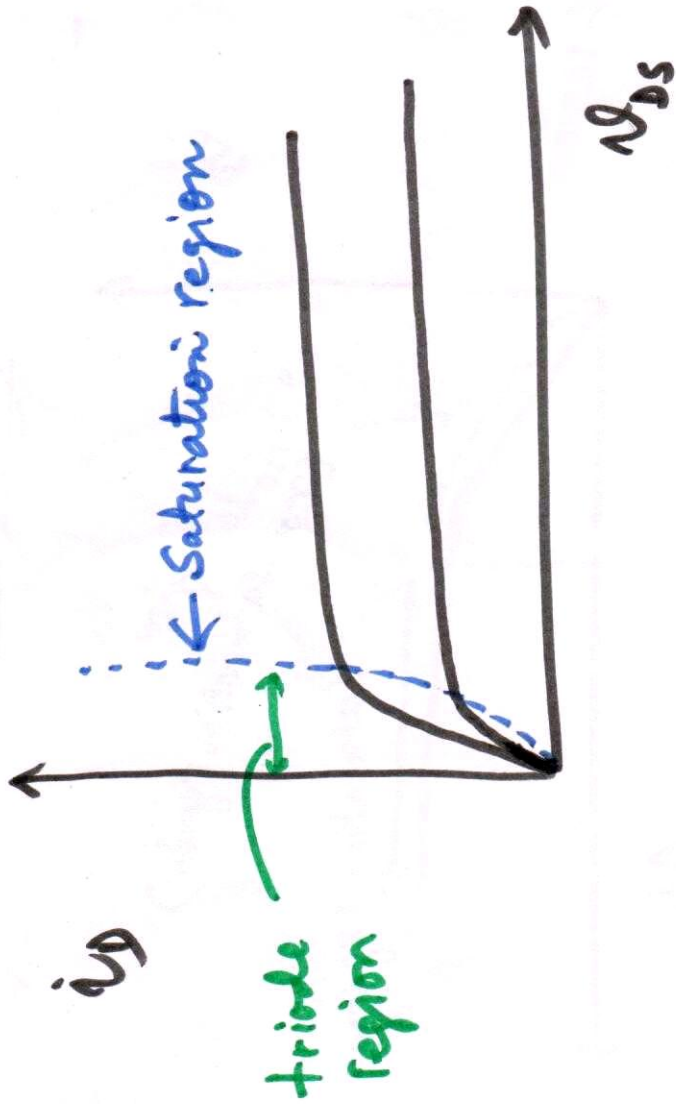Drain current becomes independent of Drain voltage



C_{ox} - Capacitance per unit area

t_{ox} - thickness of oxide layer


$\sim 50 \text{ nm}$

(SiO_2 layer)



$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$\epsilon_{ox} = \epsilon_{\text{SiO}_2} = 3.9 \epsilon_0$$
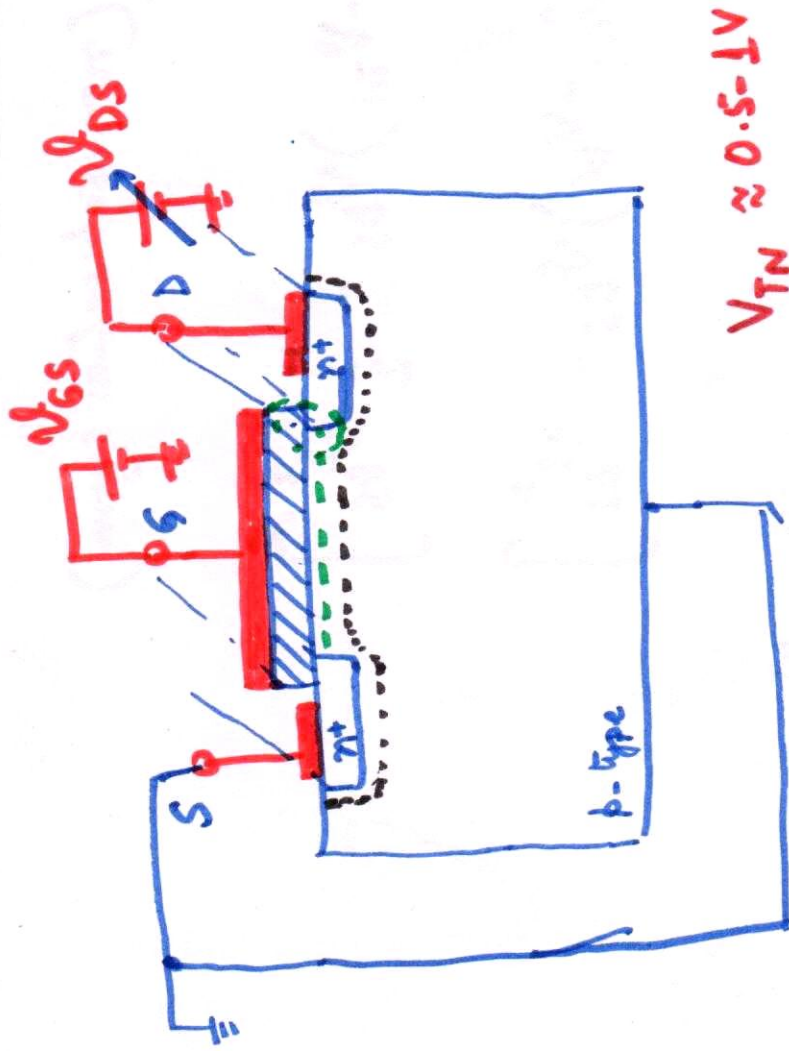
$$C_{ox} = \frac{3.9 \epsilon_0}{t_{ox}} \approx 6.9 \times 10^{-4} \text{ F/m}^2$$



NMOS

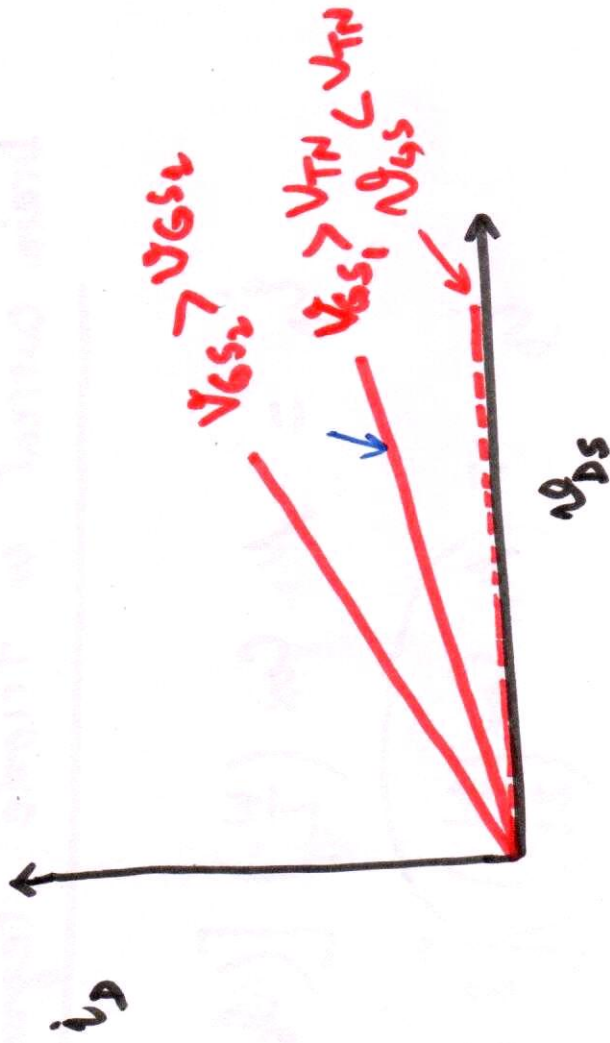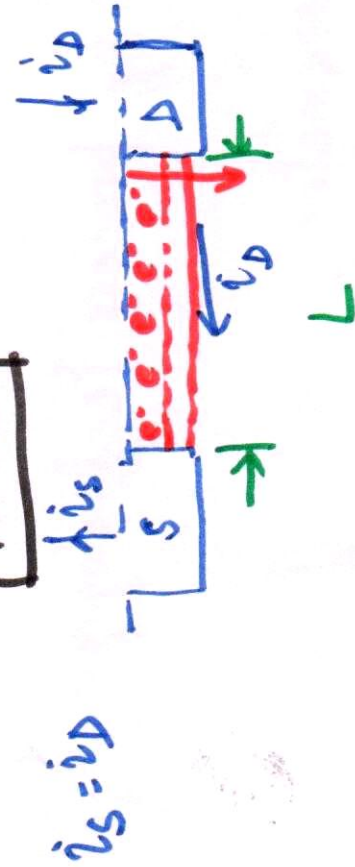

$V_{gs} = V_{TN}$ (Inversion layer is introduced)

$V_{ds} \sim mV$

Conductance of channel \propto excess voltage
($V_{gs} - V_{TN}$)

$i_d \propto (V_{gs} - V_{TN})$, also dependent on V_{ds}
or effective voltage

Overdrive Voltage

Drain current in triode region (non-saturation region)

$$i_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_{TN}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$i_D = \mu_n C_{ox} \left(\frac{W}{2L} \right) \left[2 (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2 \right]$$

Conduction parameter $K_n = \mu_n C_{ox} \frac{W}{2L}$

$\mu_n C_{ox}$: Constant \Rightarrow determined by process technology

process transconductance parameter

$$K'_n = \mu_n C_{ox} ; K_n = K'_n \left(\frac{W}{2L} \right)$$

In Saturation region

$$V_{Ds} = V_{Gs} - V_{TN}$$


$$i_D = K_n \left[2(V_{Gs} - V_{TN})^2 - (V_{Gs} - V_{TN})^2 \right]$$

$$i_D = K_n (V_{Gs} - V_{TN})^2$$

Saturation

BJT, FET \rightarrow Integrated ckt
 \uparrow
 Operational Amplifier (OP-AMP) - uses more than one transistor
 IC 741

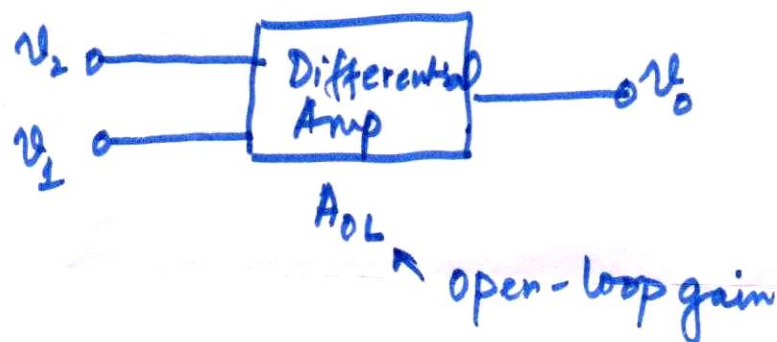• First building block - Differential Amplifier
 (most widely used block)



v_0 depends on the difference between input signals.

Ideal Output voltage, $v_0 = A_{OL}(v_1 - v_2)$

Case 1 : If $v_1 = v_2$, $v_0 = 0$

Case 2 : $v_1 = -v_2$, ———.

differential mode input voltage

$$v_d = v_1 - v_2$$

Common-mode input voltage

$$v_{cm} = \frac{v_1 + v_2}{2}$$

$$v_1 = v_2$$

$$v_d = 0, v_{cm} = v_1 = v_2$$

$$v_1 = -v_2$$

$$v_d = 2v_1, v_{cm} = 0$$

②

27/3/19

$$V_o = A_d V_d + A_{cm} V_{cm}$$

differential gain




common-mode gain

CMRR (Common Mode Rejection Ratio)

$$CMRR = \frac{A_d}{A_{cm}}$$


$$CMRR (dB) = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right)$$

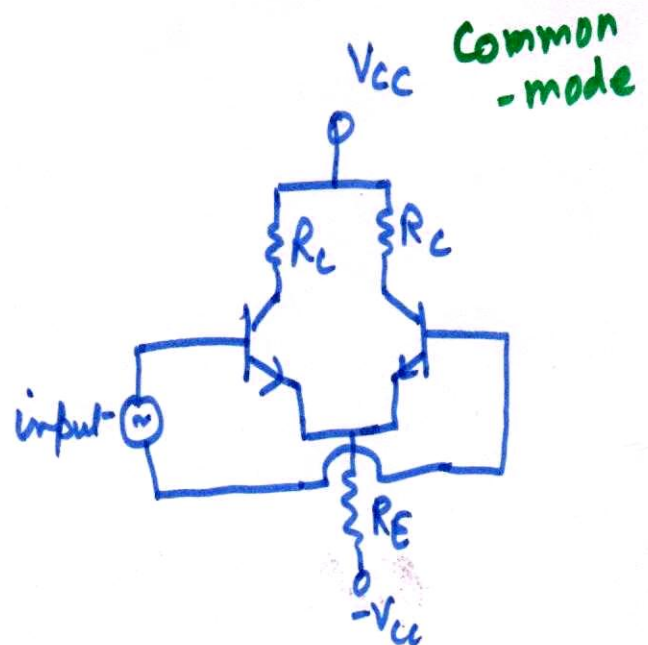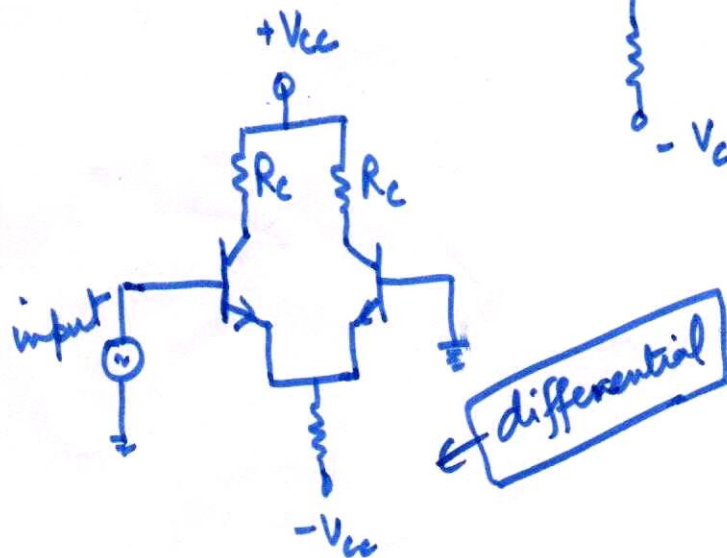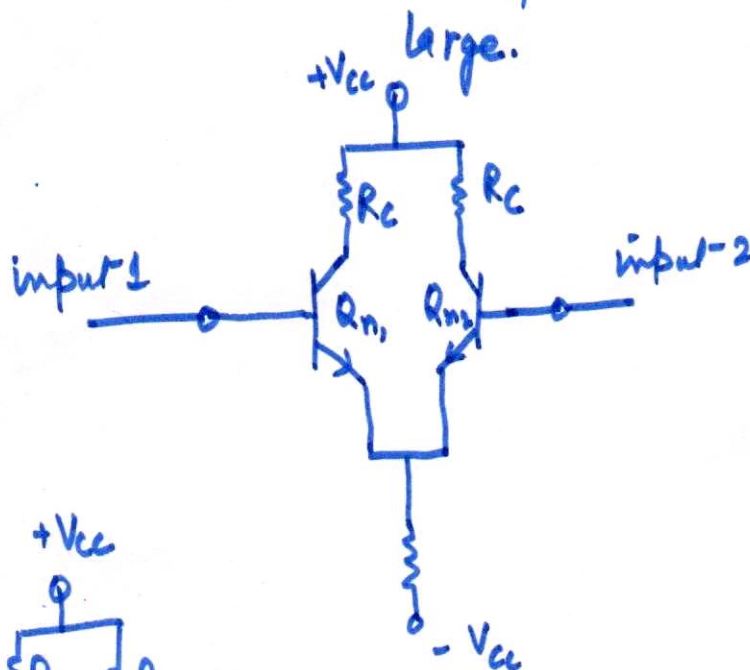$A_d \gg A_{cm}$, CMRR of the device (OP-AMP) is very large.




③ Op-amp (IC 741)


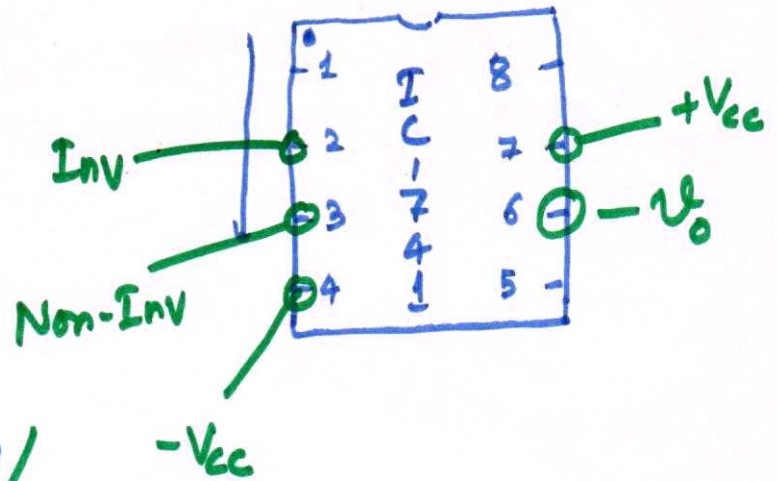
- Uses differential amplifier
- Very high gain amplifier
- High Input Impedance ($\sim M\Omega$)
- low Output Impedance
- large gain bandwidth




Inverting

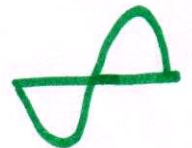

Non-inv.

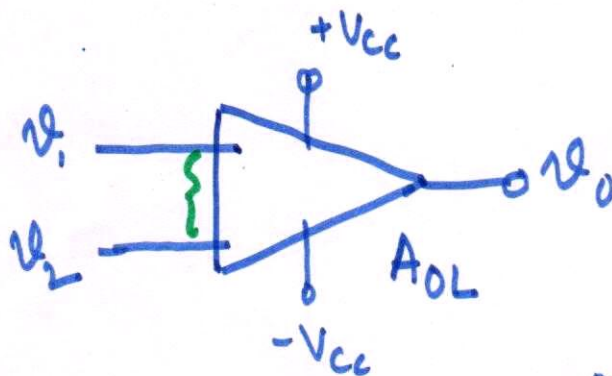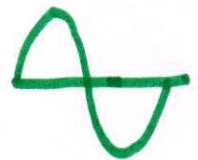


$$v_o = A_{OL} (v_1 - v_2)$$

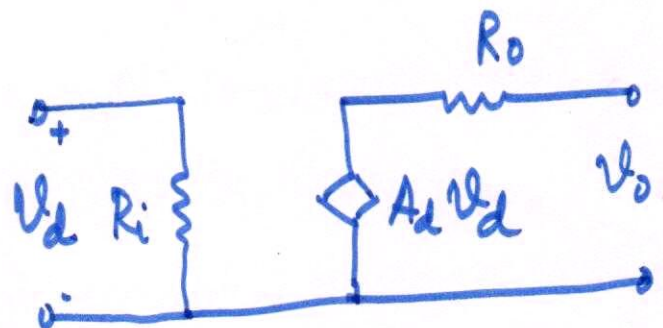

Inverting

①

1/4/19

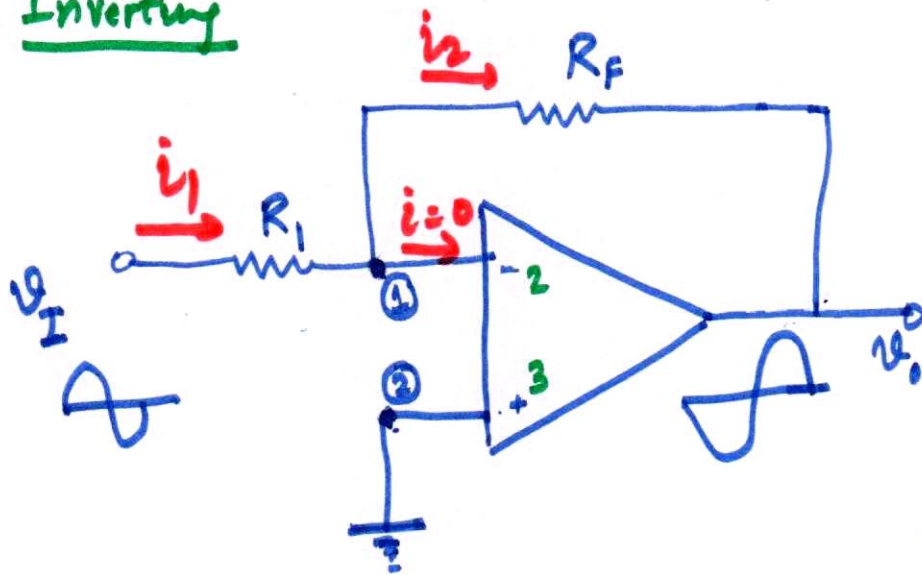

Op-amp: ideal
(open loop gain
is infinite)

$$v_o = A_{OL} (v_2 - v_1)$$

$$v_1 \rightarrow v_2$$

potential at ② $\xrightarrow{\text{same as}}$ ③
(voltage)

"Virtual ground concept"

$$\text{②} \rightarrow \text{at ground, } v_2 = 0, \quad v_1 = 0$$

$$i_1 = \frac{v_I - v_1}{R_1} = \frac{v_I}{R_1}$$

$$i_2 = i_1,$$

$$v_o = v_2 - i_2 R_F,$$

$$v_o = -\frac{v_I}{R_1} R_F \Rightarrow$$

$$\boxed{\frac{v_o}{v_I} = -\frac{R_F}{R_1}}$$

$$\text{Gain, } \frac{v_o}{v_I} = -\frac{R_F}{R_1}$$

Closed loop gain

Assume that


op-amp has finite gain A

(2)

$$v_o = A(v_2 - v_1)$$

$$v_o = A(-v_1)$$

$$\Rightarrow v_1 = -v_o/A$$

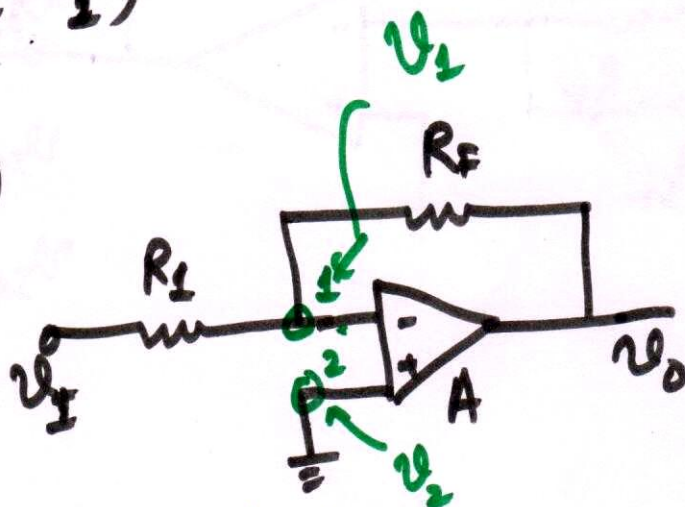

$$i_1 = \frac{v_I - v_1}{R_I} = \frac{v_I - (-v_o/A)}{R_I}$$

$$i_2 = i_1, \quad v_o = v_1 - i_2 R_F$$


$$v_o = \left(-\frac{v_o}{A}\right) - \left(\frac{v_I + v_o/A}{R_I}\right) \cdot R_F$$

\Rightarrow

$$\frac{v_o}{v_I} = \frac{-(R_F/R_I)}{\left[1 + \frac{1}{A} \left(1 + \frac{R_F}{R_I}\right)\right]}$$


Effect of
finite
gain!

(3)

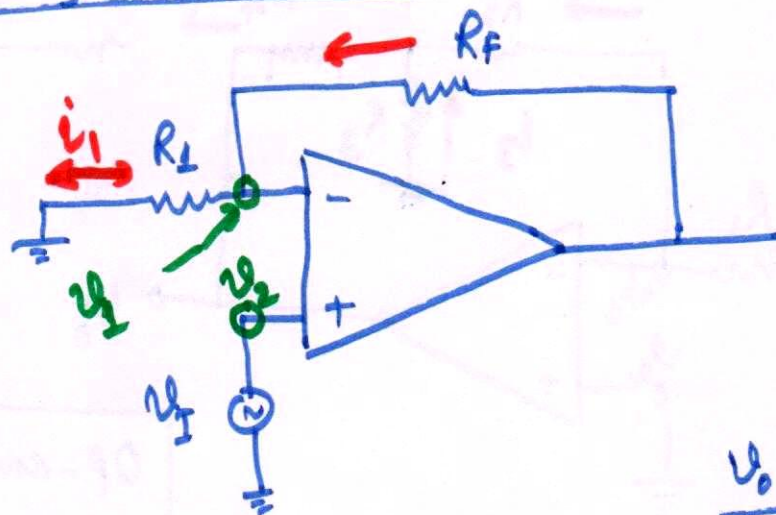Non-Inverting OP-AMPOp-amp
is ideal- Virtual
ground
concept

From the "virtual ground concept" $\frac{v_O}{v_I} = \left(1 + \frac{R_F}{R_I}\right)$


$v_1 = v_2 = v_I$

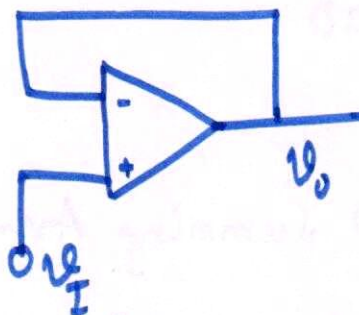Voltage
followerUnity - buffer $\frac{v_O}{v_I} = 1$

$$v_O = v_I$$

HW/Tutorial : Op-amp has finite gain .?


T-Network

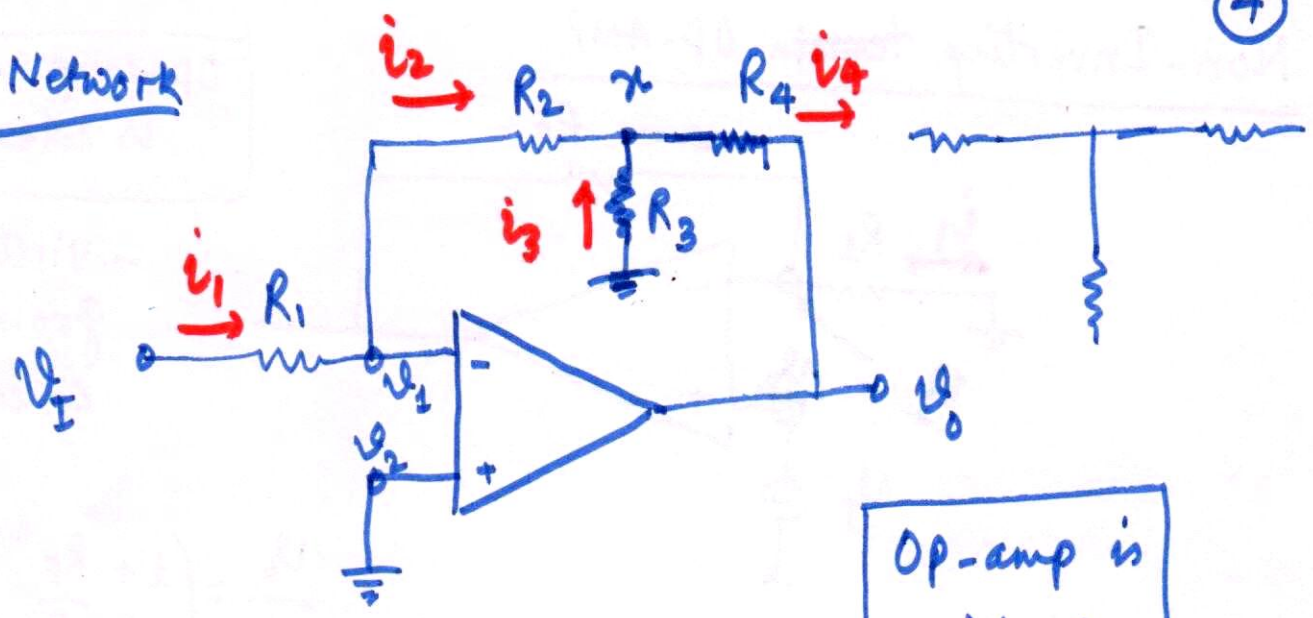

$V_O = ?$, $\frac{V_O}{V_I} = ?$

$V_1 = 0, V_2 = 0$

Adder (Weighted Summing Amplifier)

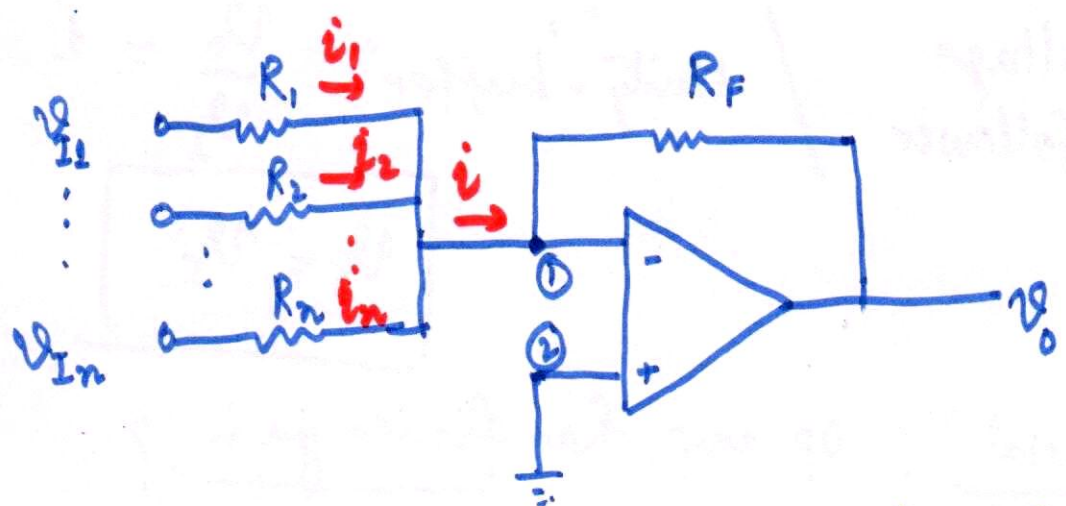



$$i = i_1 + i_2 + \dots + i_n = \frac{V_{I1}}{R_1} + \frac{V_{I2}}{R_2} + \dots + \frac{V_{In}}{R_n}$$

$V_O = -i R_F$


$V_O = -R_F (\quad)$

Tut/HW

3/4/19

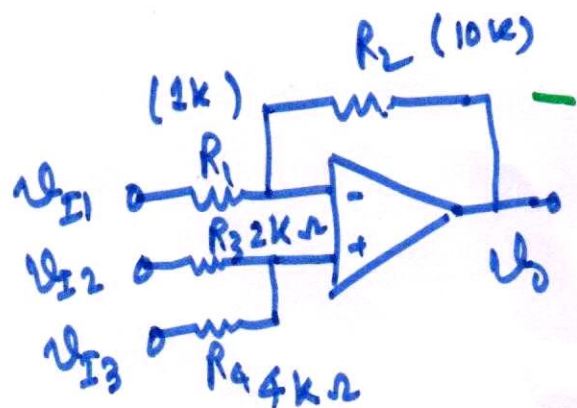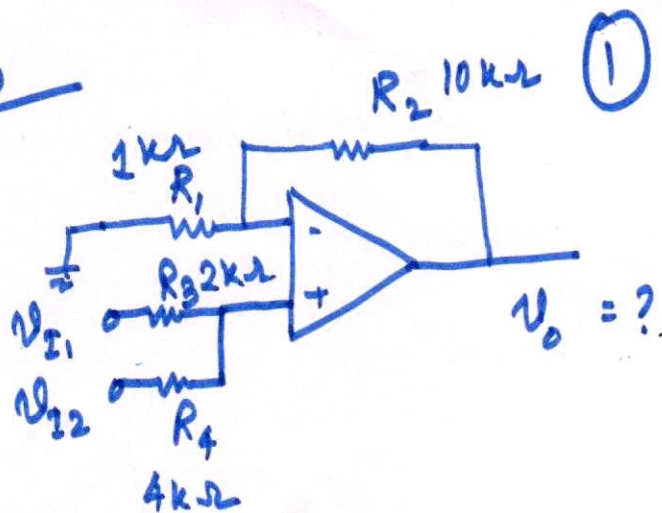

Difference Amplifier (Subtraction)

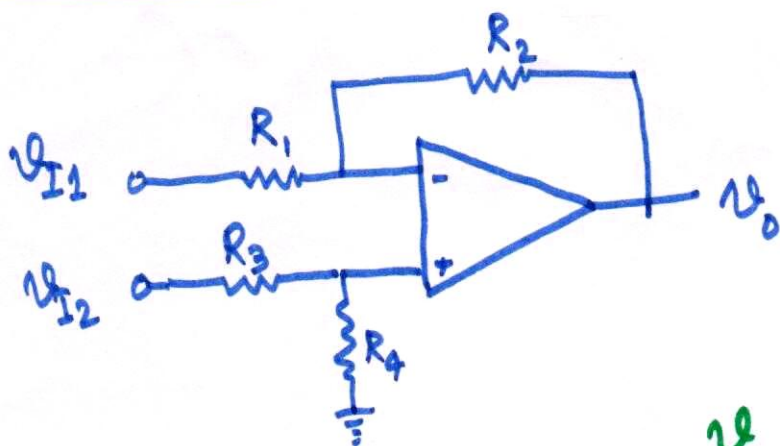

Ideal op.amp

- virtual ground
Concept



- Superposition
principle

$$V_O = V_{O1} + V_{O2}$$

V_{O1}
(V_{I2} is grounded)
 V_{I1}

(V_{I1} is grounded)
 V_{I2}
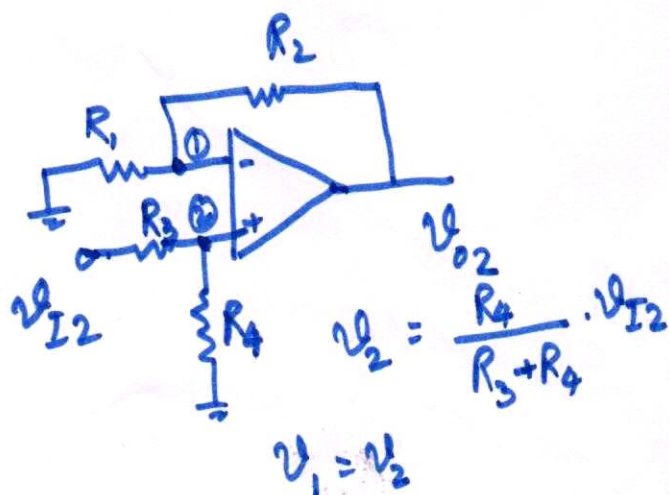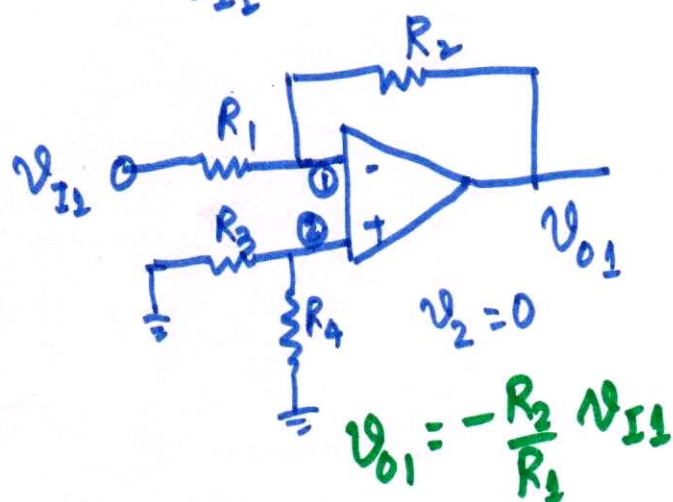
$$V_{O2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{I2}$$



$$V_o = V_{o1} + V_{o2}$$

$$V_o = -\left(\frac{R_2}{R_1}\right) V_{I1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{I2}$$

⋮

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) V_{I2} - \left(\frac{R_2}{R_1}\right) V_{I1}$$

If $V_{I1} = V_{I2}$,
common-mode

Output voltage zero



$$\Rightarrow \boxed{\frac{R_4}{R_3} = \frac{R_2}{R_1}}$$

$$V_o =$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2/R_1}{1 + R_2/R_1}\right) V_{I2} - \left(\frac{R_2}{R_1}\right) V_{I1}$$

} ideal -
opamp
difference
amplifier

If $V_{I1} \neq V_{I2}$
differential
- mode

$$\frac{R_4}{R_3} \neq \frac{R_2}{R_1}$$

$$V_{cm} = ?$$

$$V_d = ?$$

$$V_{cm} = \left(\frac{V_{I1} + V_{I2}}{2}\right)$$

$$A_{cm} = \frac{V_o}{V_{cm}}$$

$$V_o = \left(\frac{R_2}{R_1}\right) (V_{I2} - V_{I1})$$

$$V_o = A_d \cdot V_d$$

$$V_d = V_{I2} - V_{I1}$$

V_{I1}, V_{I2} ?
express V_{I1} & V_{I2} in terms of V_d, V_{cm}

$$V_{cm} = \frac{V_{I1} + V_{I2}}{2}$$

$$V_d = V_{I2} - V_{I1}$$

$$V_{I1} = ? \quad V_{cm} - V_d/2$$

$$V_{I2} = V_{cm} + V_d/2$$

$$\text{If } \frac{R_2}{R_1} = 10, \quad \frac{R_4}{R_3} = 11$$

Obtain the CMRR of the difference amplifier

$$\begin{matrix} V_d, & V_{cm}, \\ A_d, & A_{cm} \end{matrix}$$

$$CMRR = \frac{A_d}{A_{cm}}$$

$$(dB) = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right)$$

$$V_o = A_d \cdot V_d + A_{cm} V_{cm}$$


$$V_o = \left(\frac{121}{12} \right) V_{I2} - 10 V_{I1}$$

$$A_d = ?$$

$$A_{cm} = ?$$

$$CMRR = 2$$

Multi-stage Op-amps.

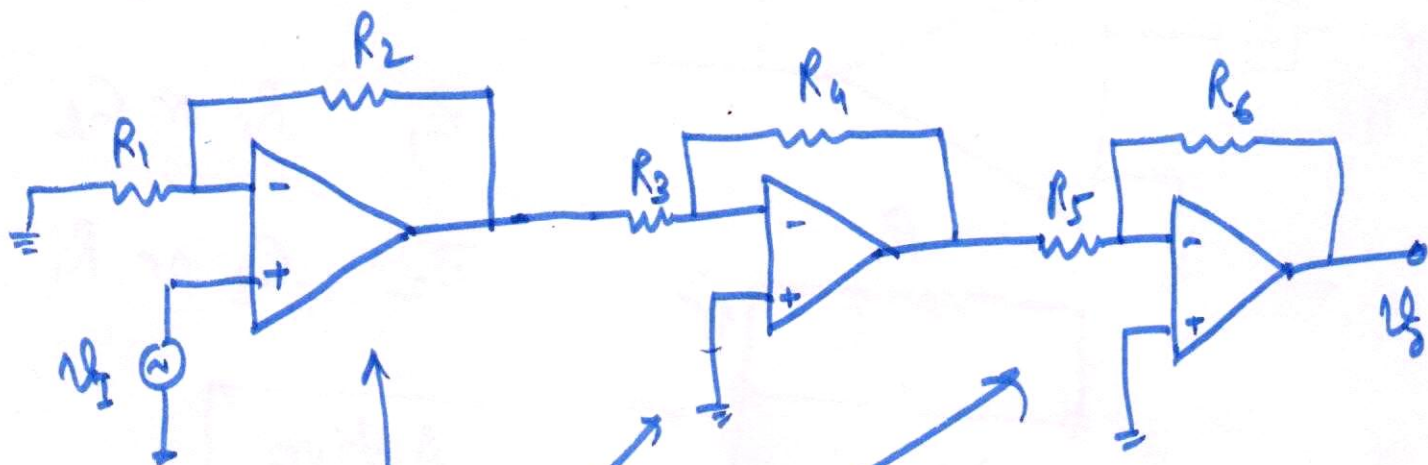

$$A = A_1 A_2 A_3$$


$A_i \rightarrow$ gain of individual op-amps

$$A_1 = \left(1 + \frac{R_2}{R_1}\right)$$

$$A_2 = -\frac{R_4}{R_3}$$

$$A_3 = -\frac{R_6}{R_5}$$

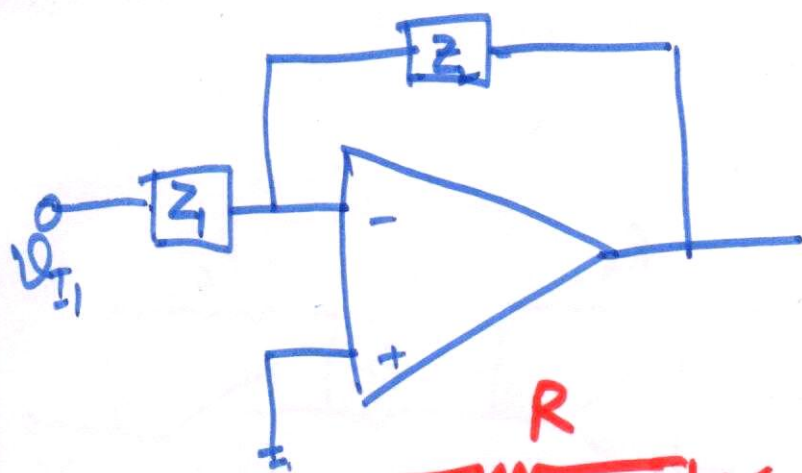
$$A = \left(\right) \left(\right) \left(\right)$$



Z_1, Z_2
impedances

Z_1 R_1 or C_1

Z_2 C_2 or R_2

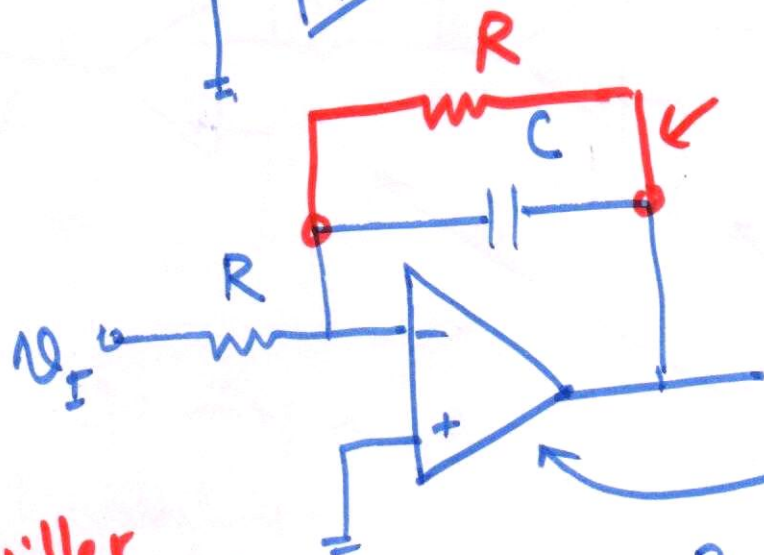


Active

Low-pass filter

Integrator

Miller Integrator

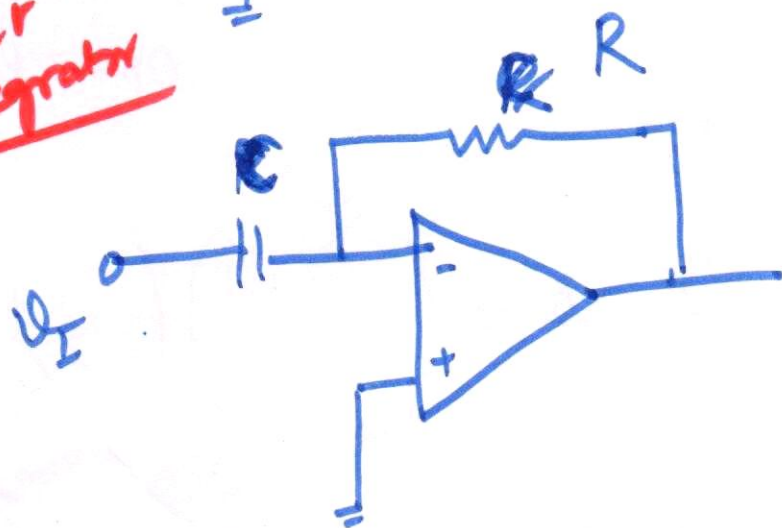

High-pass filter
Differentiator